

Chapter-I

①

Multilevel Converters

Q-1 Explain half bridge & full bridge topology of inverter with waveforms.

ANS. DC to AC converters are known as inverters.

↳ The function of an inverter is to change a DC input voltage to symmetric ac output voltage of desired magnitude and frequency.

↳ The output voltage waveforms of ideal inverters should be sinusoidal.

↳ Single phase inverters are classified in two topologies

- Half Bridge

- Full Bridge

Prof. Vishal D Devdhar

Assistant professor



Department of Electrical Engineering

Sanjaybhai Rajguru college of Engineering

②

The & &

Half Bridge Inverter

 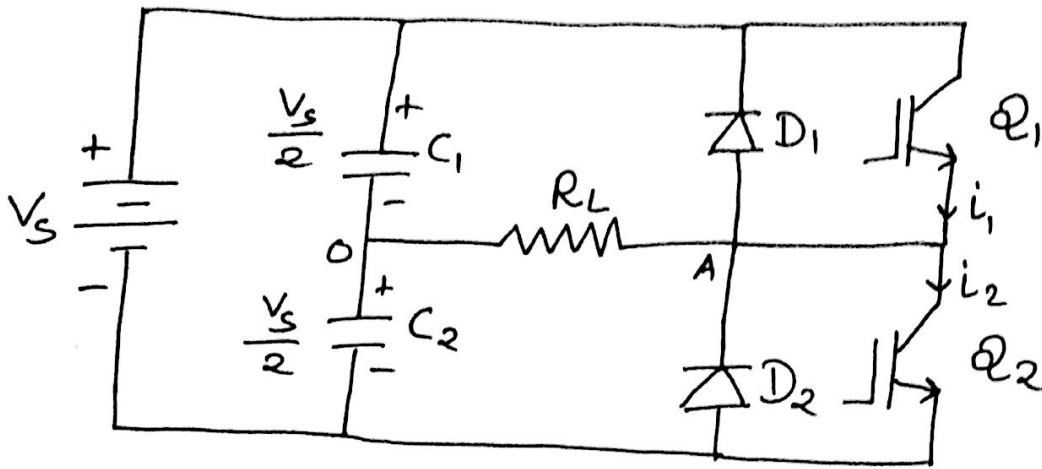

- ↳ Inverter consists two switching Q_1 & Q_2 .
- ↳ When Q_1 is ON for time $T/2$, the instantaneous voltage across the load V_o is $V_s/2$.
- ↳ When Q_2 is ON for a time $T/2$ the V_o is $-V_s/2$.

↳ The control circuit to turn ON & OFF (2)
 ϕ_1 & ϕ_2 should be designed not to fire
 ϕ_1 & ϕ_2 at same time.

↳ The root mean square (rms) output voltage

$$V_o = \sqrt{\frac{2}{T} \int_0^{T/2} \frac{V_s^2}{4} dt}$$

$$= \sqrt{\frac{2V_s^2}{4T} [t]_0^{T/2}}$$

$$= \sqrt{\frac{V_s^2}{2T} \left[\frac{T}{2} - 0 \right]}$$

$$= \sqrt{\frac{V_s^2}{4}}$$

$$\boxed{V_o = \frac{V_s}{2}}$$

Advantages

- ↳ Output voltage is half of input voltage, so when load voltage requirement is less & higher source voltage is available this converter is useful.
- ↳ Only two number of switches are used.
- ↳ Less complex control circuit.

5

- ↳ This inverter consists of four switches.
- ↳ Q_1 & Q_2 are turned on simultaneously & the input voltage V_s appears across the load.
- ↳ When Q_3 & Q_4 are turned on the voltage across the load is reversed and is $-V_s$.
- ↳ The rms output voltage V_o

$$\begin{aligned}
 V_o &= \sqrt{\frac{2}{T} \int_0^{T/2} V_s^2 dt} \\
 &= \sqrt{\frac{2V_s^2}{T} [t]_0^{T/2}} \\
 &= \sqrt{\frac{2V_s^2}{T} \left(\frac{T}{2}\right)}
 \end{aligned}$$

$V_o = V_s$

Advantages

- ↳ RMS output voltage is V_s .
- ↳ Full utilization of source.
- ↳ Requires two terminal DC source.


Disadvantages

- ↳ Four number of switches are used.
- ↳ complex control circuit.

⑥

Q-2 Discuss 180° conduction mode of 3-phase full bridge inverter.

 ANS Three phase inverters are used for high power applications (more than 10kW).




↳ In 180° conduction mode each switch conducts for 180° .

↳ At any instant of time 3 switches remain ON.


↳ When switch Q1 is on terminal a is connected to positive terminal of the input DC source.

180° Mode of conduction

(7)

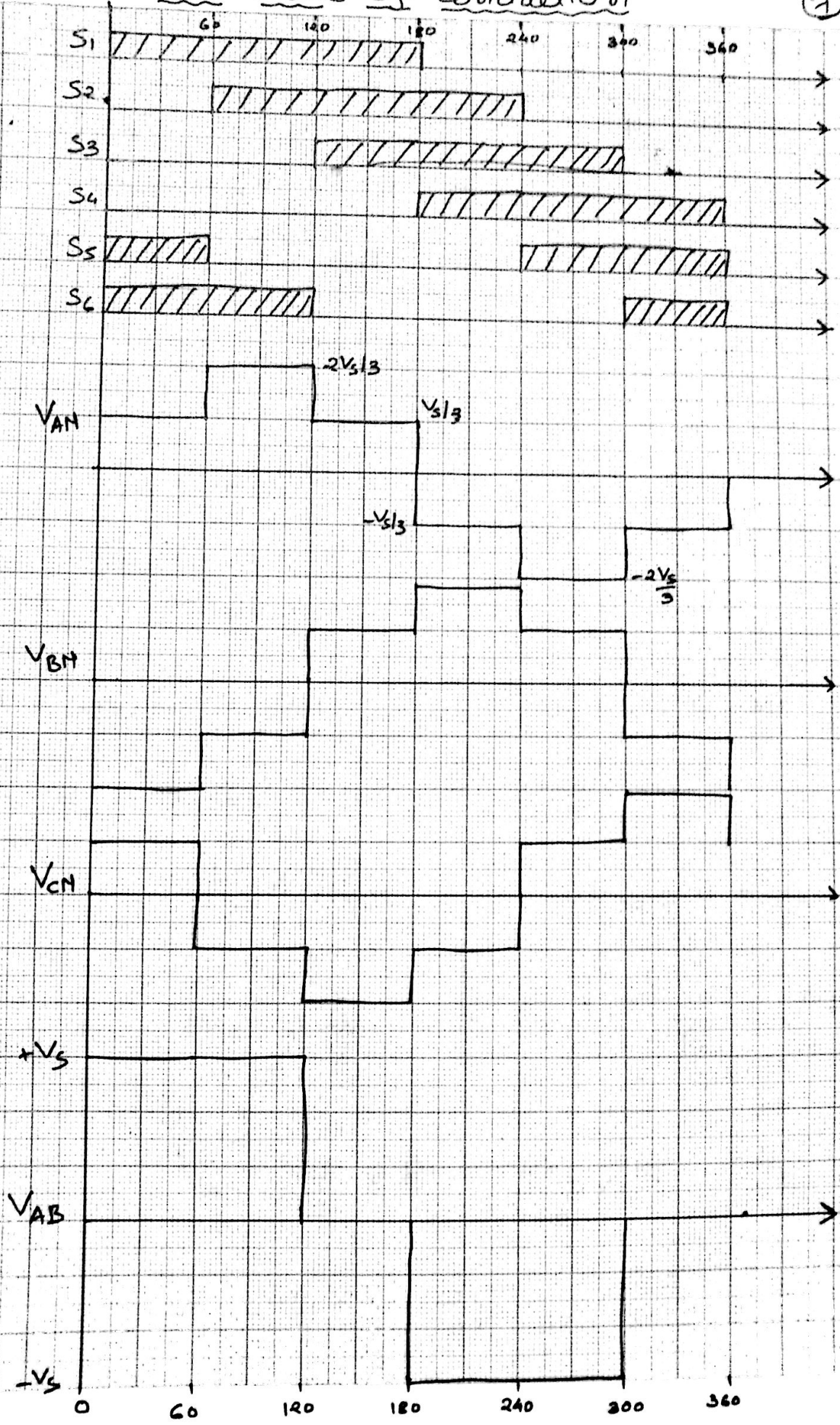

- ↳ When ~~terminal~~ switch Q_4 is on terminal a is connected to negative of DC source.
- ↳ There are six modes of operation in a cycle and duration of each mode is 60° .
- ↳ The load is connected in star.
- ↳ switches of any leg of inverter $S_1 \& S_4, S_3 \& S_6, S_5 \& S_2$ are complementary switches and can not be on simultaneously.
- ↳ Because it would result in short circuit across DC link voltage supply.
- ↳ During mode-1 switches $Q_1, Q_5 \& Q_6$ are ON
- ↳ As a result equivalent circuit

 

$$R_{eq} = R + \frac{R}{2} = \frac{3R}{2}$$

$$i_1 = \frac{V_s}{R_{eq}} = \frac{2V_s}{3R}$$

$$\therefore V_{AN} = i_1 \times R = \frac{2V_s}{3R} \times R = \frac{2V_s}{3}$$

$$V_{BN} = -i_1 \times R = -\frac{2V_s}{3R} \times R = -\frac{2V_s}{3}$$

$$V_{CN} = \frac{i_1}{2} \times R = \frac{2V_s}{2 \times 3R} \times R = \frac{V_s}{3}$$

④

↳ Similarly for all mode we can find the value of phase voltages.

↳ All phase voltages at every mode is shown in the wave form.

↳ The value of line voltages can be find

by $V_{AB} = V_{AN} - V_{BN}$

for mode-I

$$V_{AN} = \frac{V_s}{3}$$

$$V_{BN} = -\frac{2V_s}{3}$$

$$V_{AB} = V_{AN} - V_{BN}$$


$$= \frac{V_s}{3} - \left(-\frac{2V_s}{3}\right)$$

$$= \frac{V_s}{3} + \frac{2V_s}{3}$$

$$\underline{V_{AB} = V_s}$$

120° Mode of conduction

(10)

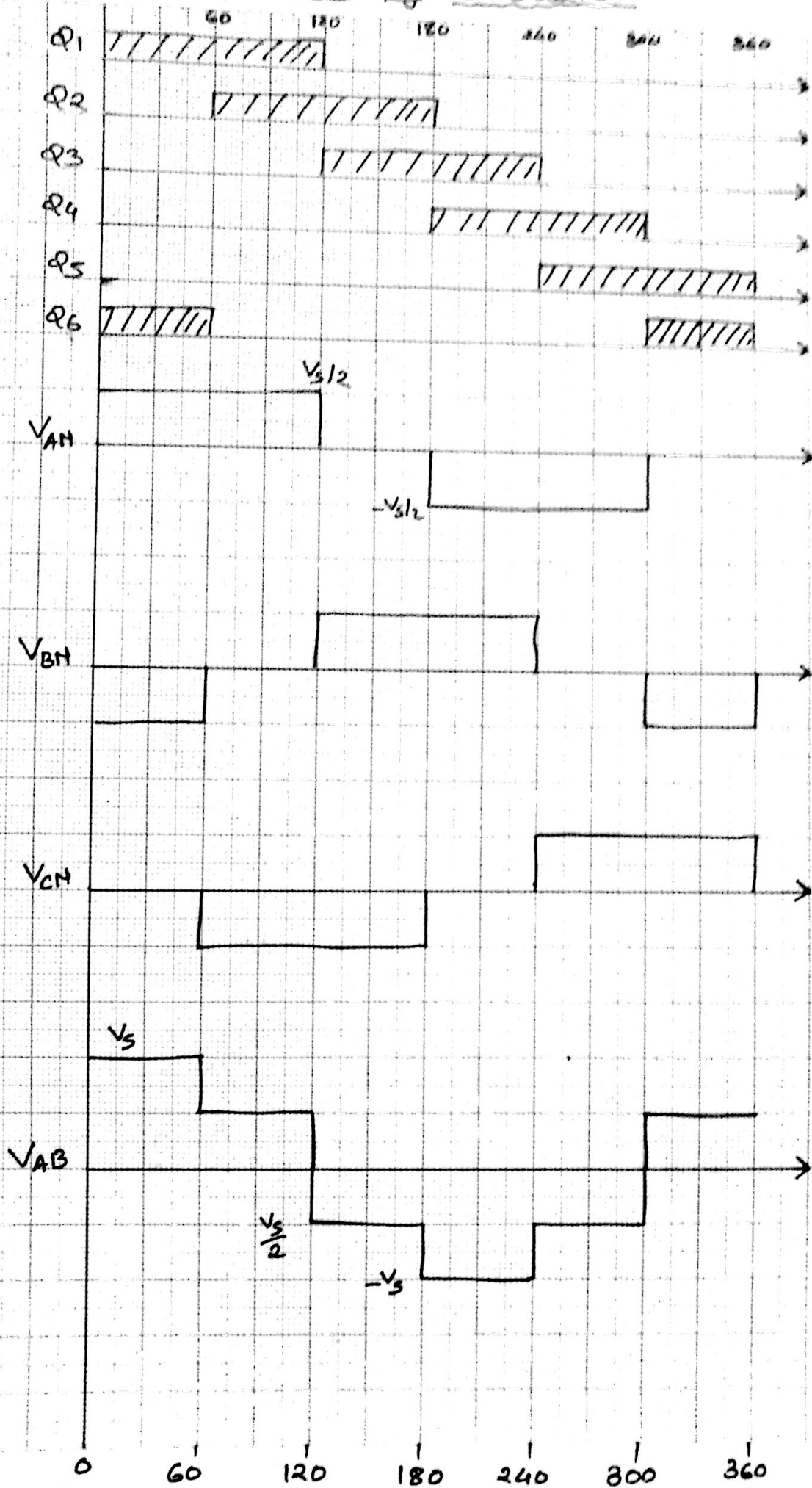

Q-3 Discuss 120° mode of conduction of 3-phase inverter. (11)

ANS. Power circuit for 120° conduction & 180° conduction is same.


↳ The each switch conducts for 120° so the name is 120° conduction mode.

↳ In this configuration at a time only two switches are on.

↳ Each ~~switch~~ Interval between two adjacent switches is 60° .

↳ During mode-I switches ~~Q_1~~ & Q_6 are ON.

↳ The equivalent circuit during mode-I

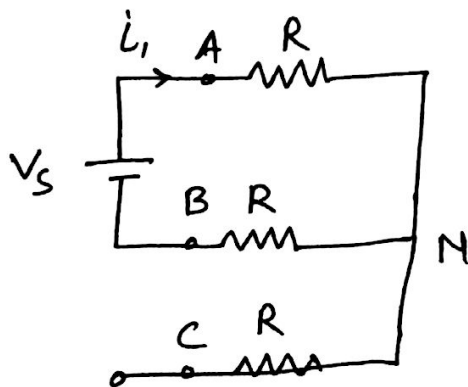

$$i = \frac{V_s}{2R}$$

$$V_{AN} = i \times R = \frac{V_s}{2R} \times R = \frac{V_s}{2}$$

$$V_{BN} = -i \times R = -\frac{V_s}{2R} \times R = -\frac{V_s}{2}$$

$$V_{CN} = 0$$

$$\begin{aligned} V_{AB} &= V_{AN} - V_{BN} \\ &= \frac{V_s}{2} - \left(-\frac{V_s}{2}\right) \end{aligned}$$

$V_{AB} = V_s$ As shown in waveforms.

(12)

Q-4 What are the features of Multilevel Inverters? Explain each in detail.

ANS. Two level inverter produce square wave output voltage waveform which contains harmonics.

- ↳ Multilevel inverter produce quasi-~~square~~^{sine} wave or nearly ~~square~~ sine wave voltage output.
- ↳ Multilevel inverter generates the o/p voltage waveforms with more steps of smaller magnitude.
- ↳ It is possible to use low voltage rating power semiconductor device for multilevel inverter due to small voltage steps of o/p voltage.
- ↳ In multilevel inverter it is possible to obtain refined output voltage waveforms with increased number of voltage level & reduced THD in voltage.
- ↳ It is possible to obtain machine currents with reduced harmonics, resulting into reduced torque pulsation in the drive system.

- ↳ By reducing magnitude of each voltage step with increment in number of level it is possible to reduce dv/dt . (13)
- ↳ By reduction in dv/dt , voltage stress on insulation is less.
- ↳ With lower switching frequency of operation electromagnetic interference (EMI) is reduced.
- ↳ Lower magnitude of common mode voltage (CMV) and in motor drive low value of bearing current flows.
- ↳ As switching frequency is reduced the switching losses are also very less.

(14) Q-5 classify multilevel inverter and write down the applications of multilevel inverter. 2-6

ANS. The multilevel inverters are classified in major three categories as follows.

- ↳ Neutral point clamped (Diode clamped)
- ↳ Flying capacitor
- ↳ ~~the~~ H-Bridge inverter
 - Symmetrical H-Bridge
 - Asymmetrical H-Bridge

Applications of Multilevel Inverters.

- ↳ High power, high voltage adjustable speed drives (ASD)
- ↳ Luminators
- ↳ Rolling mills
- ↳ conveyors
- ↳ compressors
- ↳ Pumps
- ↳ fans
- ↳ Marine
- ↳ Blowers

Q-6 Explain Neutral Point clamped 3-level inverter with switching table, circuit diagram and relevant waveforms. (15)

ANS. In this topology of multilevel inverter the DC link is split into number of small voltage levels using a bank of series connected bulk-capacitors.


↳ The inverter structure allows the connections of the inverter poles to any one of these voltage levels thus generating a multi-level voltage waveform.

↳ In this inverter topology middle point O of the two DC link capacitors C_1 & C_2 is defined as a Neutral point.

↳ Here as the mid voltage level is formed by clamping the switching devices to the neutral-point of the DC-bus.

↳ Each leg of the inverter consists of four switches and two diodes (clamping diodes).

16

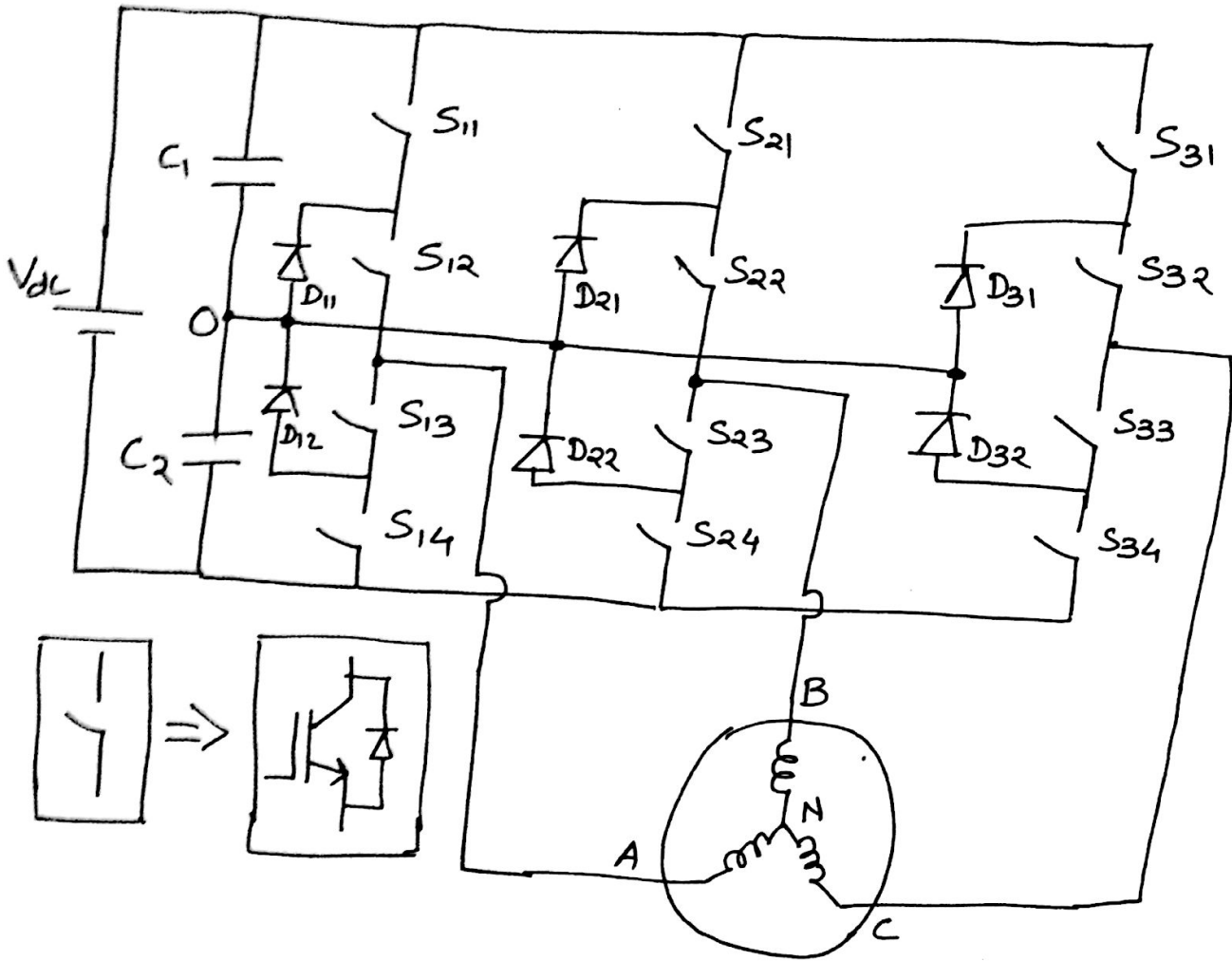


Pole voltage V_{AO}	S_{11}	S_{12}	S_{23}	S_{24}
$+\frac{V_{DC}}{2}$	1	1	0	0
0	0	1	1	0
$-\frac{V_{DC}}{2}$	0	0	1	1

S_{11} & S_{13} } complementary
 S_{12} & S_{14} }

1 \Rightarrow ON state
 0 \Rightarrow OFF state

 Vishal D Devdhar
Assistant Professor (Elect.)
Sanjaybhai Rajguru college of
Engineering (SRCE), Rajkot.



Pole voltage V_{A0}

↳ Each pole of this inverter can attain one of the three voltage levels

$$+\frac{V_{DC}}{2}, 0 \text{ \& } -\frac{V_{DC}}{2}$$

with respect to neutral point O.

↳ Pole voltage V_{A0} attains the level of $V_{DC}/2$ when top switches S_{11} & S_{12} are ON.



↳ Level $-V_{DC}/2$ is realized when the bottom switches S_{13} & S_{14} are turned ON.

↳ Zero voltage level is obtained when inner two switches S_{12} & S_{13} are turned ON and the V_{A0} gets clamped to the neutral point through Diodes D_{11} & D_{12} depending on the direction of the load current.

Q-7 Discuss 3-level flying capacitor inverter topology in detail.

ANS. In this topology of multilevel inverter there ~~are~~ is a one capacitor which acts as a floating source of energy change to $\frac{V_{DC}}{2}$.

- ↳ This circuit is called flying capacitor (capacitor clamped) multilevel inverter.
- ↳ As independent capacitor clamp the device voltage to one capacitor voltage level.
- ↳ In this configuration the capacitor can be kept charged to half the DC-link voltage and the capacitor voltage can be added or subtracted from the DC-link voltage to generate more levels at the output pole of the inverter.
- ↳ Inverter consists of four switches and a capacitor connected between inner two switches as shown in circuit diagram.

 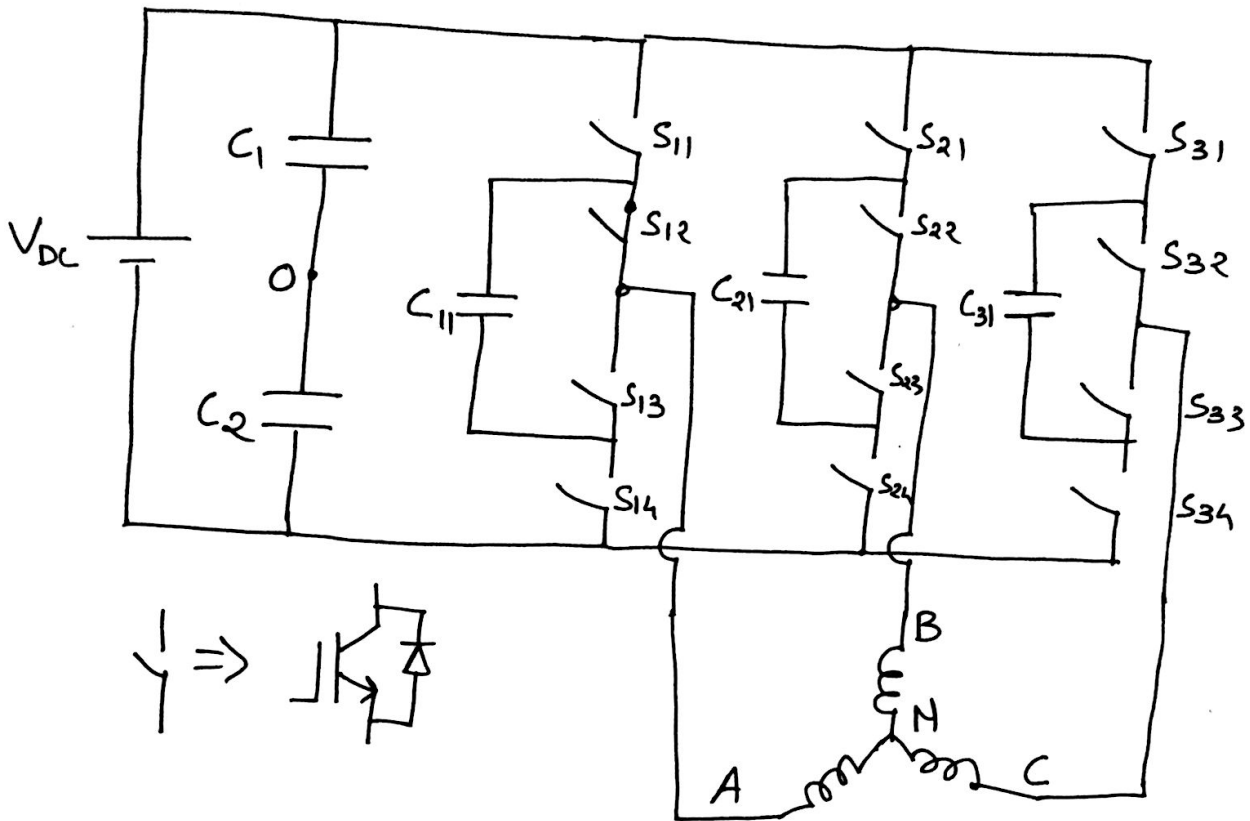


Pole voltage V_{AO}	S_{11}	S_{12}	S_{13}	S_{14}	C_{11}
$V_{DC}/2$	1	1	0	0	No effect
Zero level	1	0	1	0	charging
	0	1	0	1	discharging
$-V_{DC}/2$	0	0	1	1	No effect

S_{11} & S_{14} } Complementary
 S_{12} & S_{13} } Pair of switches

$1 \Rightarrow$ ON state
 $0 \Rightarrow$ OFF state

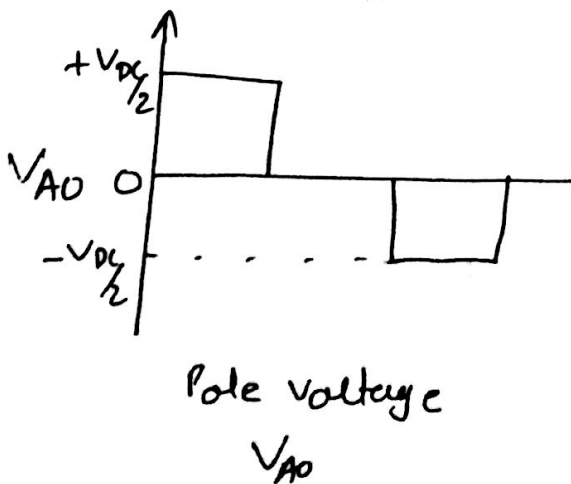(20)

- ↳ When switches S_{11} & S_{12} are ON, the output pole voltage V_{AO} is $+V_{DC}/2$.
- ↳ Pole voltage level $-V_{DC}/2$ is obtained when bottom switches S_{13} & S_{14} are turned ON.
- ↳ Zero voltage level can be attained by two switching states.
- ↳ S_{11} & S_{13} are turned ON capacitor C_{11} is charging and $+V_{DC}/2$ voltage is subtracted from the DC-link voltage which is $V_{DC}/2$ and hence zero voltage level appears.
- ↳ Switches S_{12} & S_{14} are turned ON and capacitor C_{11} is discharging and voltage $-V_{DC}/2$ is added to the DC-link voltage $V_{DC}/2$ and zero voltage level is attained.



Q-8 Explain the DC voltage balance

(21)

techniques for capacitor clamped multilevel inverters.

ANS. Flying capacitor topology has two different switching state for zero voltage level.

↳ This is called redundancy.

↳ The availability of voltage redundancies allows controlling the individual capacitor voltages.

↳ To produce the same output voltage, the inverter has different combinations of capacitor charging or discharging.

↳ This flexibility makes it easier to manipulate the capacitor voltages and keep them at their proper values.

↳ It is possible to make individual capacitor to charge or discharge by selection of proper switching state.

↳ Thus by proper selection of switching capacitor voltage can be balanced.

(22)


Q-9 Explain different H-bridge topology of multilevel inverter. Write down advantages and disadvantages of the H-bridge topology over other inverter topology.

ANS. H-Bridge inverter topology is the most popular converter topologies used in high-power medium voltage drives.

- ↳ It is composed of a multiple units of single phase H-bridge power cells.
- ↳ The H-bridge cells are normally connected in cascade on their all side to achieve medium-voltage operation and low harmonic distortion.
- ↳ This topology requires a number of isolated DC supplies each of which feeds an H-bridge power cell.
- ↳ There are mainly two H-bridge topology are there.
 - ↳ Symmetric topology
 - ↳ Asymmetric topology


↳ Symmetric

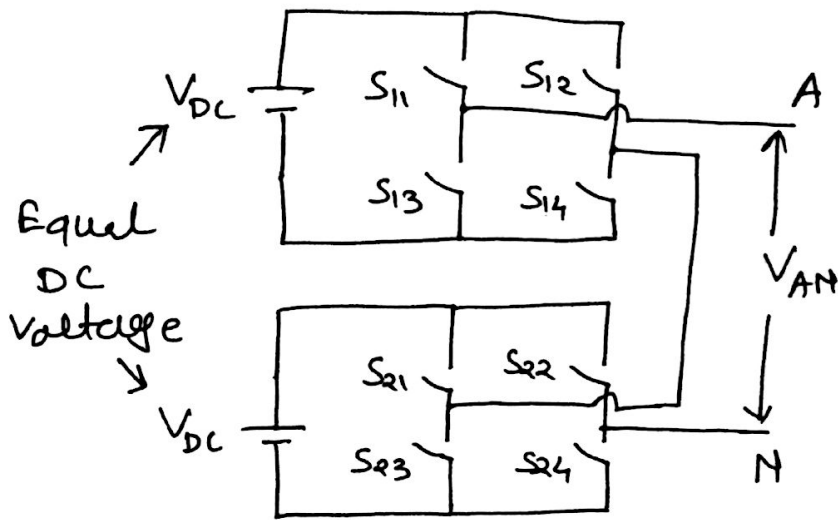↳ In symmetric topology each power cell is powered by an isolated DC supply of equal voltage. V_{DC}



↳ Asymmetric

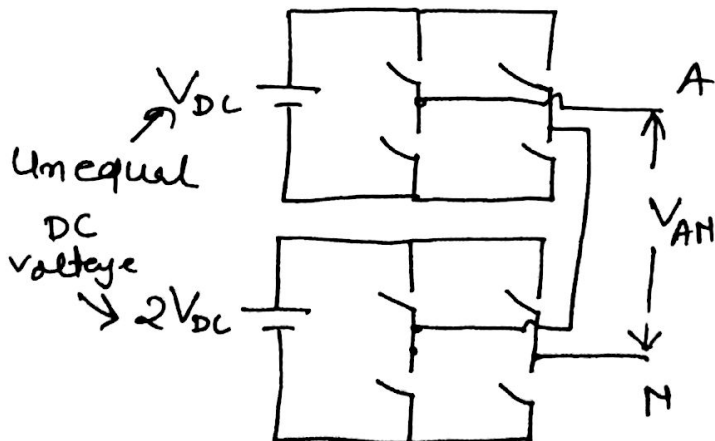↳ Asymmetric topology consists of unequal voltage of isolated DC supply to power each power cell.



(24)

Advantages

↳ Modular structure:-

This topology is composed of multiple units of identical H-bridge power cells, which leads to reduction in manufacturing cost.

↳ Low THD:-

The inverter voltage waveform is formed by a several voltage levels with small voltage steps, so inverter o/p voltage waveform is very near to a sine wave.

↳ Low dv/dt :-

As small number of voltage steps forms inverter o/p voltage, dv/dt is very less compared to other inverter topology.

↳ High-voltage operation without switching device in series:

More number of power cell compose high inverter output voltage.

Disadvantages

(25)

↳ Large number of dc supplies:-

Each power cell requires a isolated dc power supply.

↳ Large number of switches are required.