

# Multipulse Converter



[www.vishaldevdhar.org](http://www.vishaldevdhar.org)

**Vishal D Devdhar**

**Lecturer**

**Electrical Engineering Department**

**Government Polytechnic, Rajkot**

# Contents

---

- ❑ Introduction
- ❑ Advantages
- ❑ Disadvantages
- ❑ Classification:
  - Series type
  - Separate type
- ❑ Six-pulse diode rectifier
- ❑ 12-pulse diode rectifier

# Introduction

---

- ❑ The rectifiers can be configured as 12-, 18- and 24-pulse rectifiers, powered by a phase shifting transformer with a number of secondary windings.
- ❑ Each secondary winding feeds a six-pulse diode rectifier.
- ❑ The dc output of the six-pulse rectifiers is connected to a voltage source inverter.

# Advantages

---

- Ability to reduce the line current harmonic distortion
- low-order harmonic currents generated by the six-pulse rectifiers are canceled through Phase-shifting transformer
- does not require any LC filters or power factor compensators
- Phase-shifting transformer provides an effective means to block common-mode voltages

# Disadvantages

---

- ❑ Requires phase shifting transformer
- ❑ Higher the No. of pulses, increased transformer cost
- ❑ More No. of semiconductor devices are used

# Classification

---


## □ Series type multipulse rectifier

- All six pulse rectifier are connected in series at DC side
- Medium power ASD as front end converter
- NPC inverter

## □ Separate type multipulse rectifier

- Each six pulse rectifier feeds a separate DC load
- H-Bridge inverter

# Six-pulse Diode Rectifier

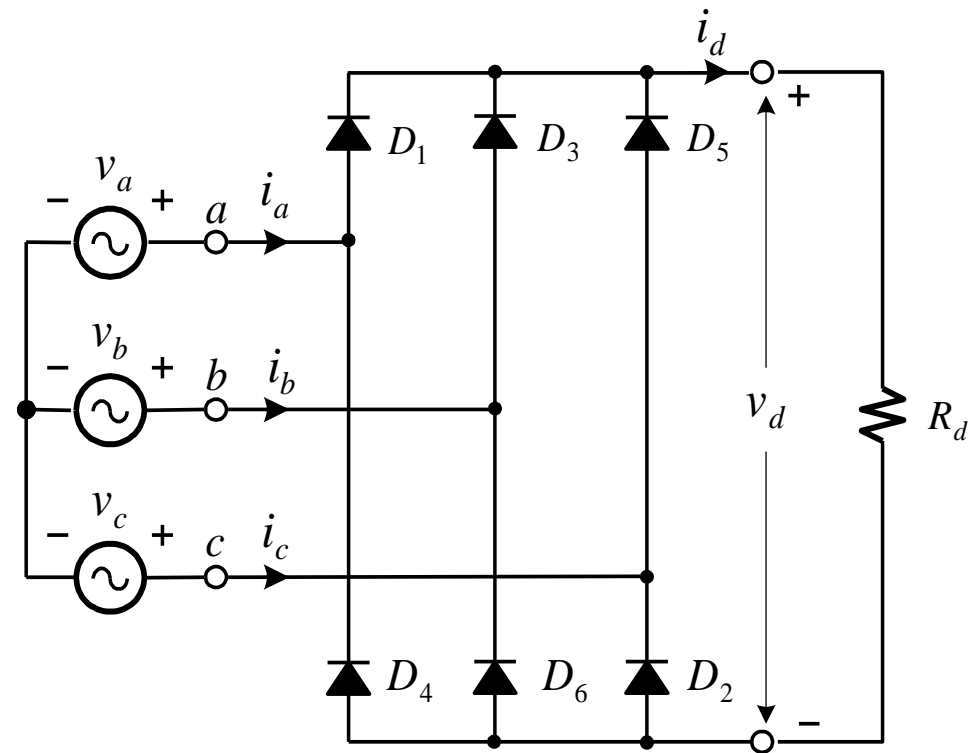

Supply Voltages:

$$v_a = \sqrt{2} V_{PH} \sin(\omega t)$$


$$v_b = \sqrt{2} V_{PH} \sin(\omega t - 2\pi/3)$$

$$v_c = \sqrt{2} V_{PH} \sin(\omega t - 4\pi/3)$$

$$v_{ab} = v_a - v_b = \sqrt{2} V_{LL} \sin(\omega t + \pi/6)$$

# Six-pulse Diode Rectifier

## Waveforms

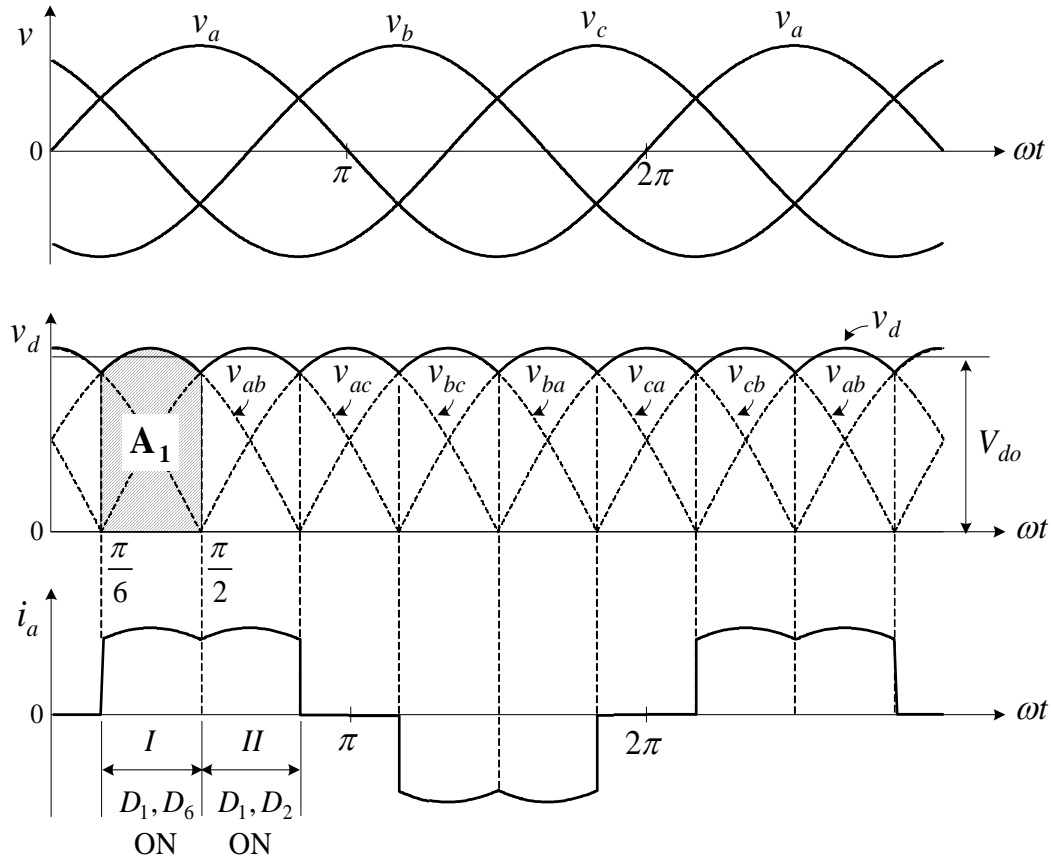

$$V_{do} = \frac{\text{area } A_1}{\pi/3} = \frac{1}{\pi/3} \int_{\pi/6}^{\pi/2} \sqrt{2} V_{LL} \sin(\omega t + \pi/6) d(\omega t) = \frac{3\sqrt{2}}{\pi} V_{LL} \approx 1.35 V_{LL}$$

[www.vishaldevdhar.org](http://www.vishaldevdhar.org)



# Six-pulse Diode Rectifier

---

- Definition of Power Factor (PF)

Per-phase average (real) power: 
$$P = \frac{1}{2\pi} \int_0^{2\pi} v_a \times i_a d(\omega t) = V_a I_{a1} \cos \phi_1$$

Per-phase apparent power: 
$$S = V_a I_a$$

Total power factor (PF): 
$$PF = \frac{P}{S} = \frac{V_a I_{a1} \cos \phi_1}{V_a I_a} = \frac{I_{a1}}{I_a} \cos \phi_1 = DF \times DPF$$

Distortion factor (DF): 
$$DF = I_{a1} / I_a$$

Displacement power factor (DPF): 
$$DPF = \cos \phi_1$$

PF =  $f$ (THD): 
$$PF = \frac{DPF}{\sqrt{1 + THD^2}}$$

# Six-pulse Diode Rectifier

---

- Per Unit System

Rated power, rated line-to-line voltage:  $S_R, V_R$


Base voltage and frequency:  $V_B = \frac{V_R}{\sqrt{3}}$  and  $\omega_B = 2\pi f_1$

Base current and impedance:  $I_B = \frac{S_R}{3V_B}$  and  $Z_B = \frac{V_B}{I_B}$ .


Base inductance and capacitance:  $L_B = \frac{Z_B}{\omega_B}$  and  $C_B = \frac{1}{\omega_B Z_B}$

# Six-pulse Diode Rectifier

- Typical Waveforms / Harmonic Content

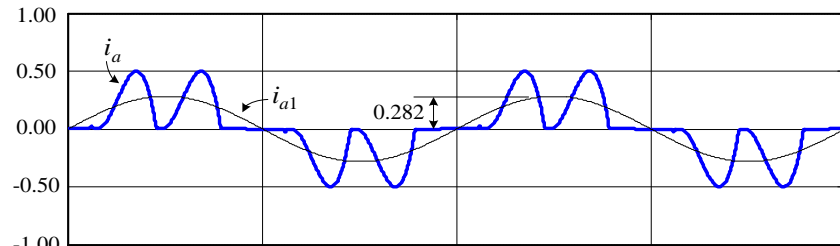

(a)  $I_{a1} = 0.2$  pu

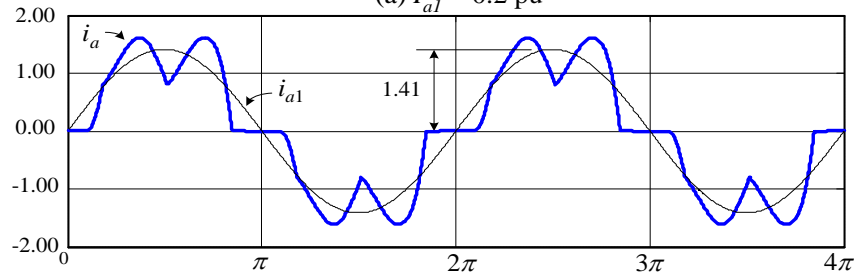


(b)  $I_{a1} = 1$  pu

Harmonics $n$	5	7	11	13	17	19	23	25	THD (%)
$I_{an} / I_{a1}$ (%) $I_{a1} = 0.2$ pu	63.4	38.7	8.99	8.64	4.22	3.61	2.48	2.02	75.7
$I_{an} / I_{a1}$ (%) $I_{a1} = 1$ pu	30.4	8.79	6.31	3.40	2.30	1.89	1.04	1.03	32.7

# 12-pulse Diode Rectifier

- Rectifier Topology

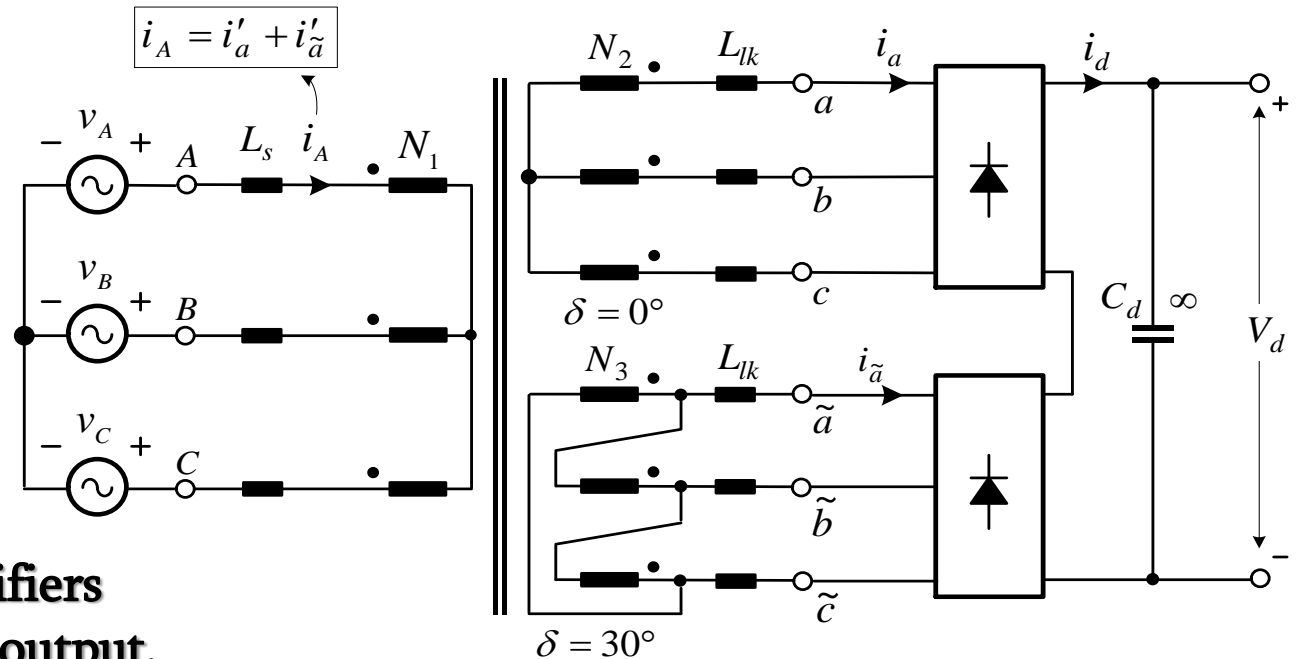


- Series type:  
Two six-pulse rectifiers are in series at the output.

- Phase shifting transformer:  $\delta = \angle V_{\tilde{a}\tilde{b}} - \angle V_{AB} = 30^\circ$


- Secondary line-to-line voltage:  $V_{ab} = V_{\tilde{a}\tilde{b}} = V_{AB} / 2$

- Turns ratio:  $\frac{N_1}{N_2} = 2$  and  $\frac{N_1}{N_3} = \frac{2}{\sqrt{3}}$ .

# 12-pulse Diode Rectifier

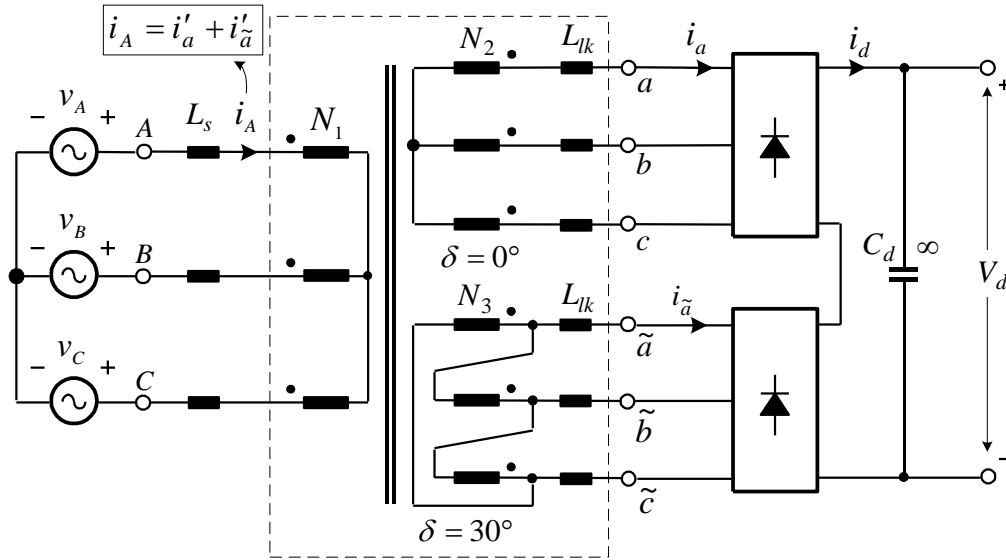







(a) 12-pulse diode rectifier

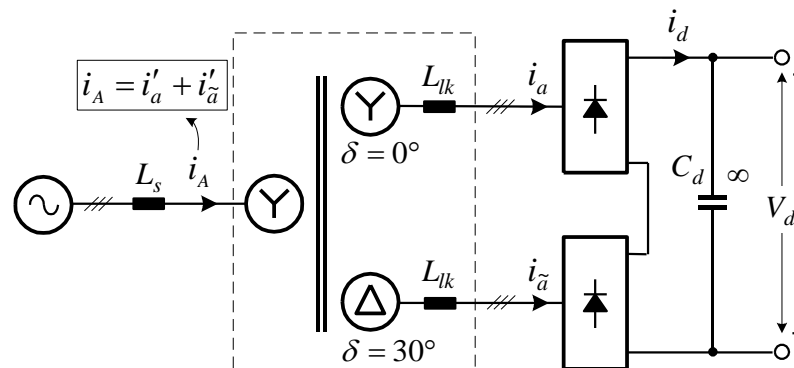

(b) Simplified diagram

# 12-pulse Diode Rectifier


## • Waveforms and FFT

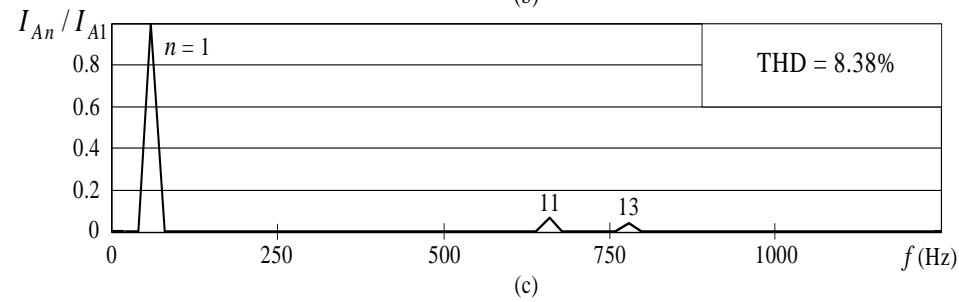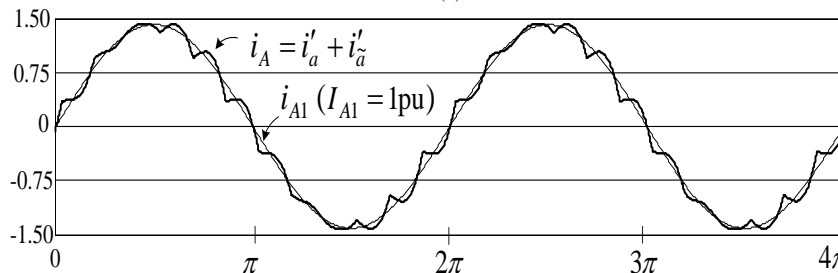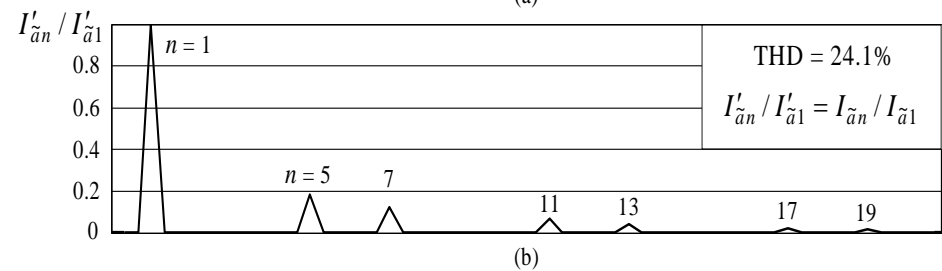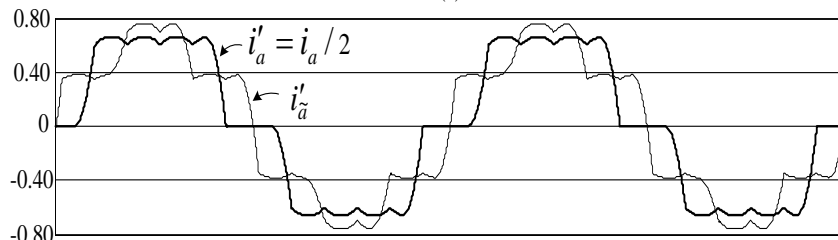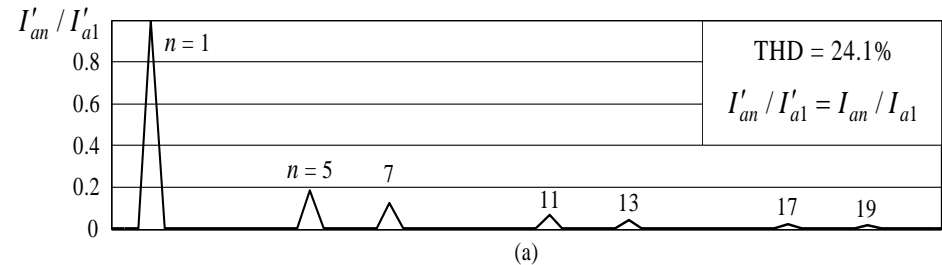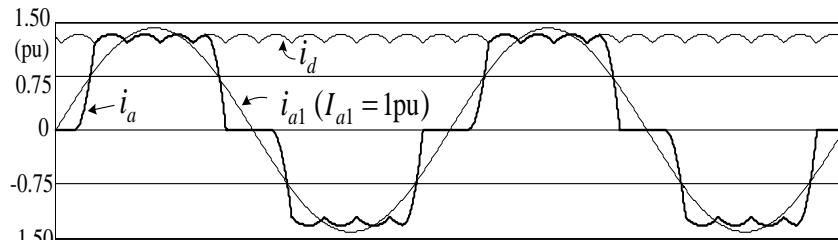

- No 5<sup>th</sup> or 7<sup>th</sup> harmonics in the line current.
- Primary line current THD: 8.38%


# Phase Shifting Transformer

- Transformer Connection Y/Z1

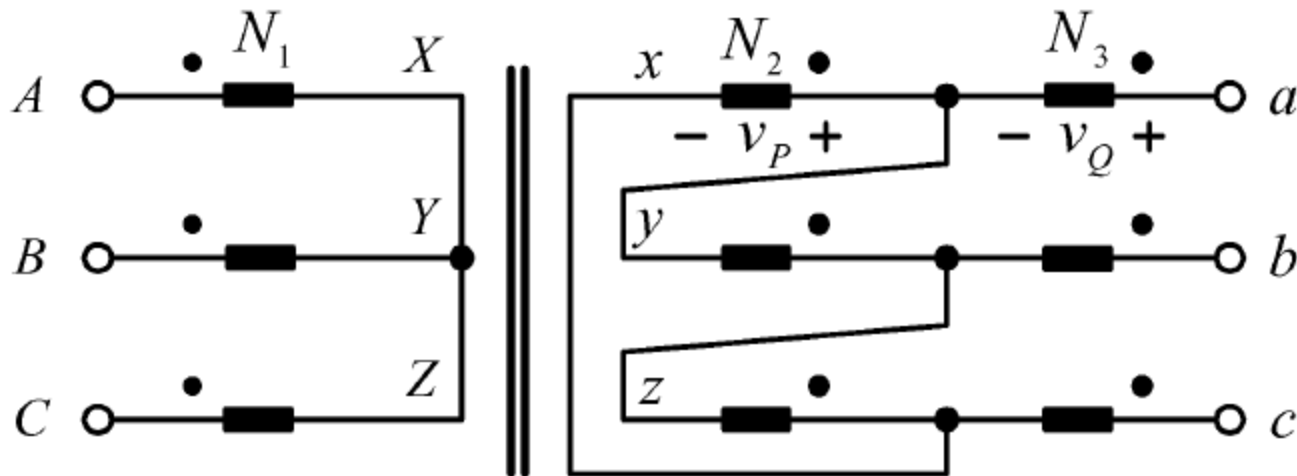

# Phase Shifting Transformer

- Transformer Connection Y/Z2

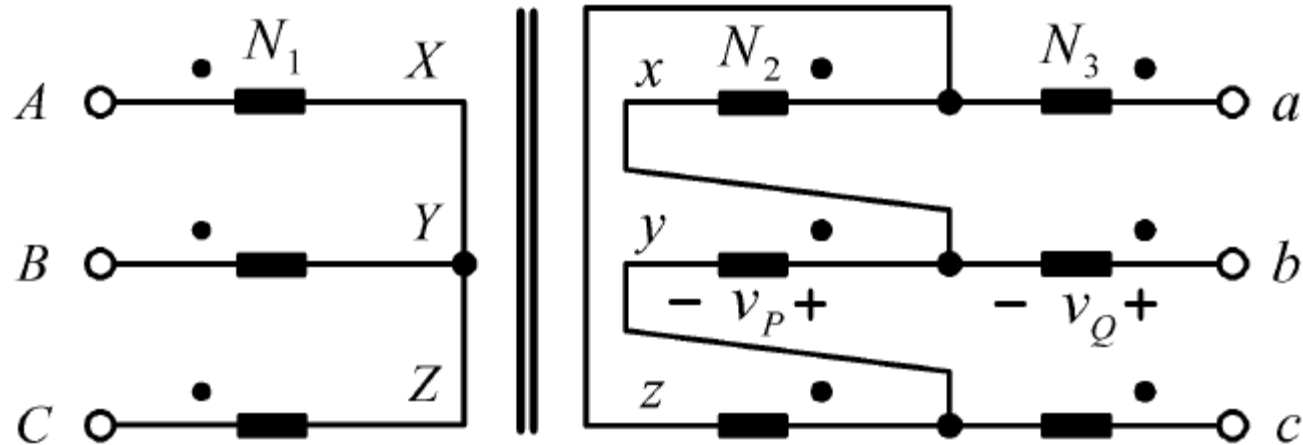




# Phase Shifting Transformer

$\delta$		$\frac{N_3}{N_2 + N_3}$	$\frac{N_1}{N_2 + N_3}$	Applications
$(\angle \bar{V}_{ab} - \angle \bar{V}_{AB})$				
Y/Z-1	Y/Z-2			
$0^\circ$	$0^\circ$	1.0	$1.0 \frac{V_{AB}}{V_{ab}}$	12-, 18-, and 24-pulse rectifiers
$15^\circ$	$-15^\circ$	0.366	$0.707 \frac{V_{AB}}{V_{ab}}$	24-pulse rectifiers
$20^\circ$	$-20^\circ$	0.227	$0.653 \frac{V_{AB}}{V_{ab}}$	18-pulse rectifiers
$30^\circ$	$-30^\circ$	0	$0.577 \frac{V_{AB}}{V_{ab}}$	12- and 24-pulse rectifiers

$\frac{V_{AB}}{V_{ab}} = 2, 3, \text{ and } 4$  for 12-, 18-, and 24-pulse rectifiers, respectively.

# 18-pulse Diode Rectifier


- Rectifier Topology

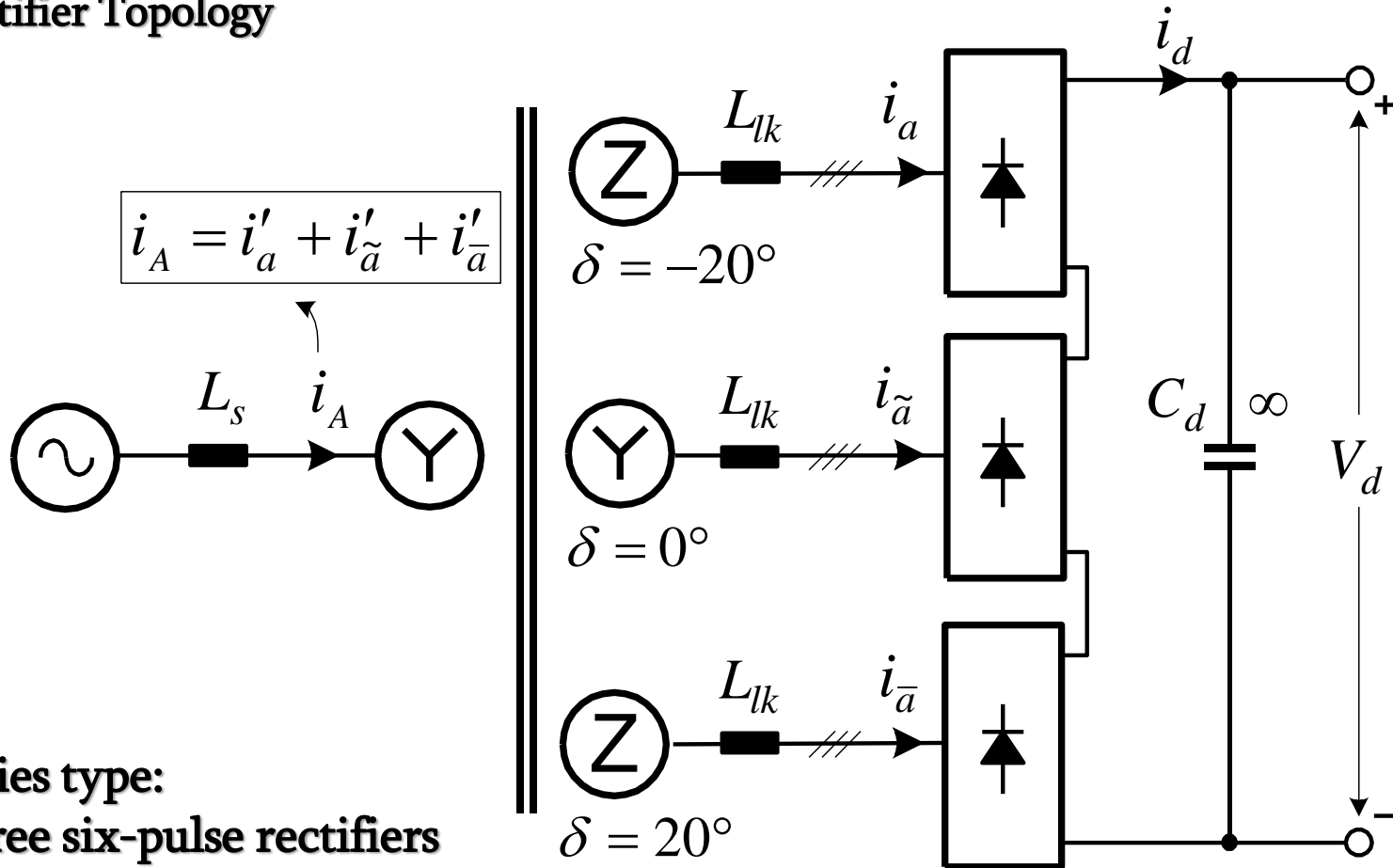

- Series type:  
Three six-pulse rectifiers  
are in series at the output.

# 18-pulse Diode Rectifier


## • Simulated Waveforms

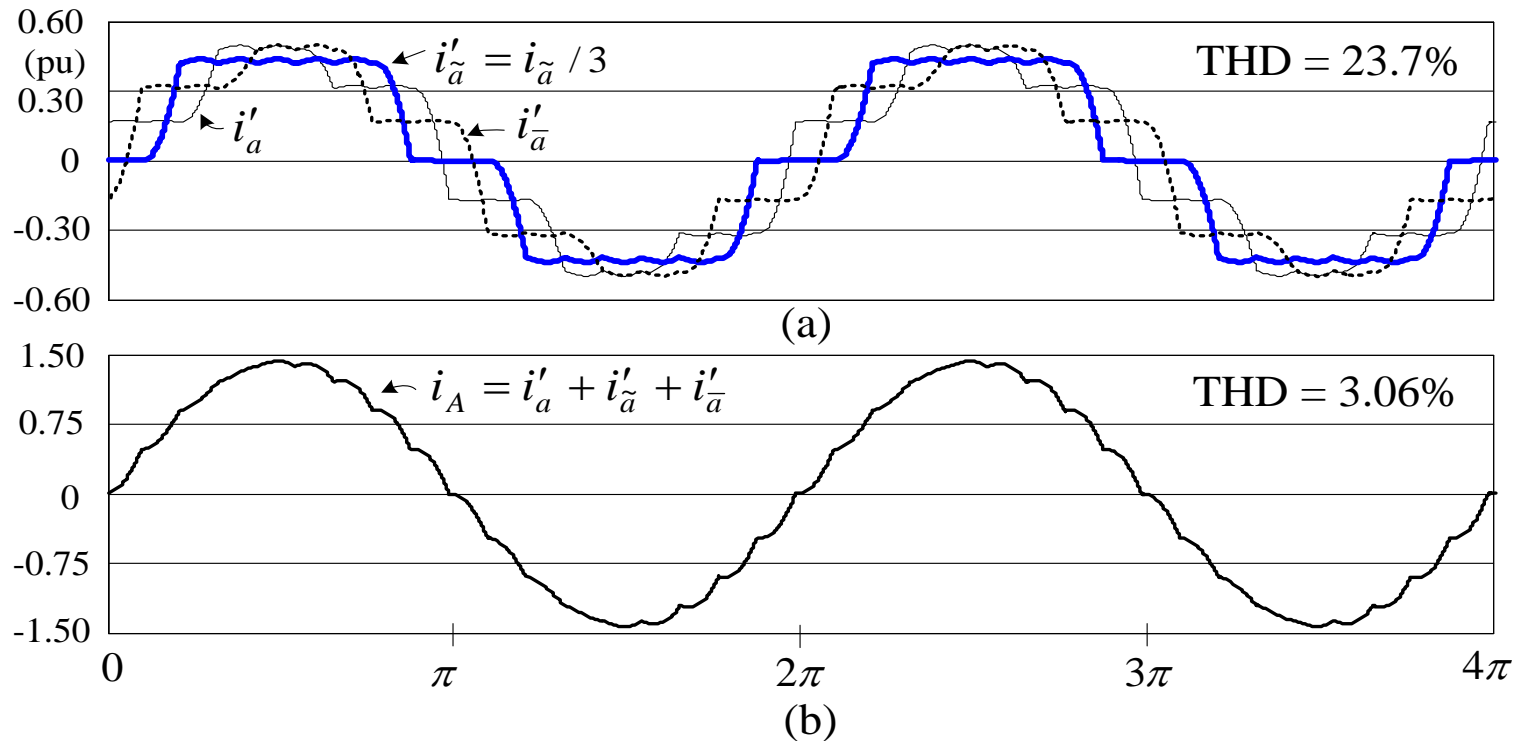


- No 5<sup>th</sup>, 7<sup>th</sup>, 11<sup>th</sup>, or 13<sup>th</sup> harmonics in the line current.
- Lowest harmonic: 17<sup>th</sup>
- Line current THD: 3.06%

# 18-pulse Diode Rectifier

- Measured Waveforms

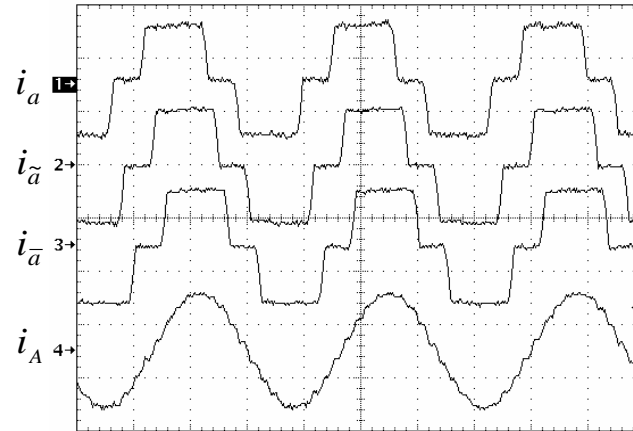

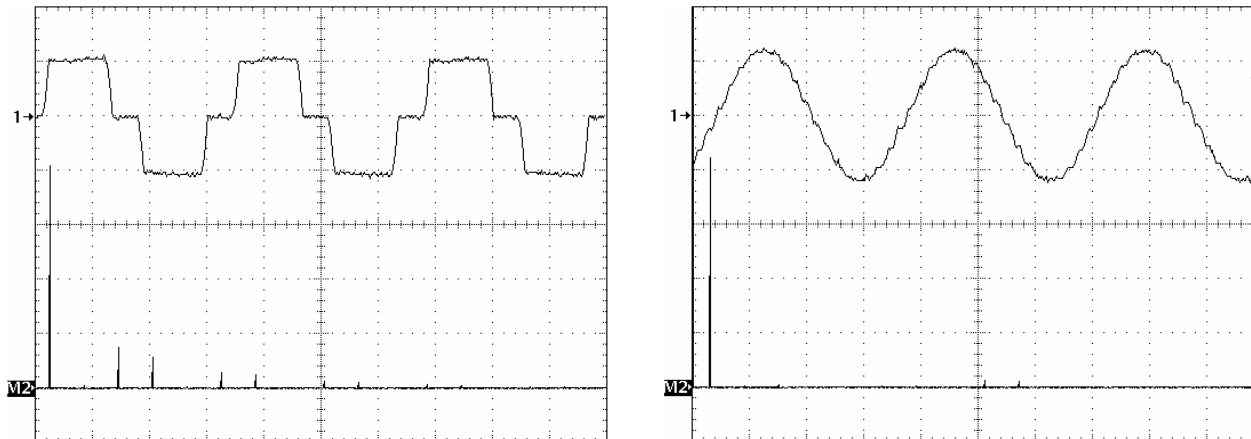
(a) Currents:  $\sqrt{2}$  pu/div, 5ms/div



(b) Spectrum:  $\sqrt{2}/5$  pu/div, 200Hz/div


# 24-pulse Diode Rectifier

- Rectifier Topology

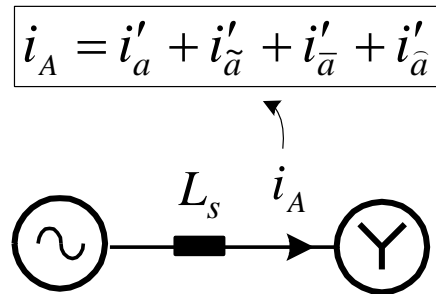


- Series type:  
Four six-pulse rectifiers  
are in series at the output.

Phase-Shifting :(Zigzag) Transformer

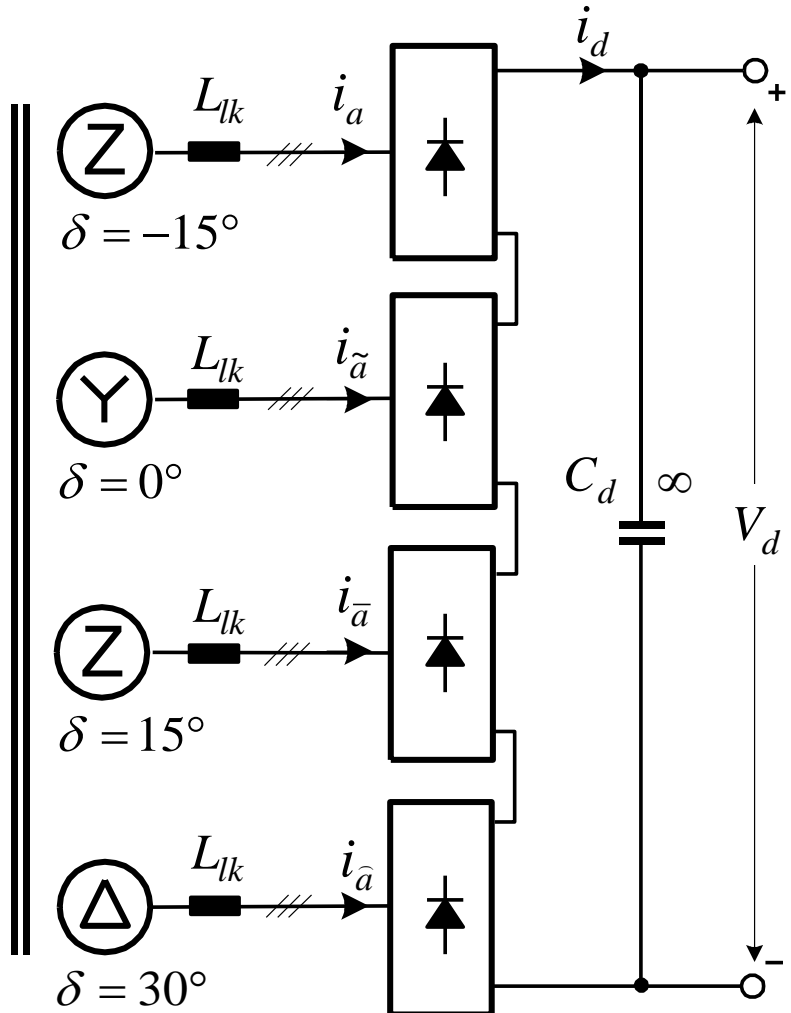


# 24-pulse Diode Rectifier

- Typical Waveforms

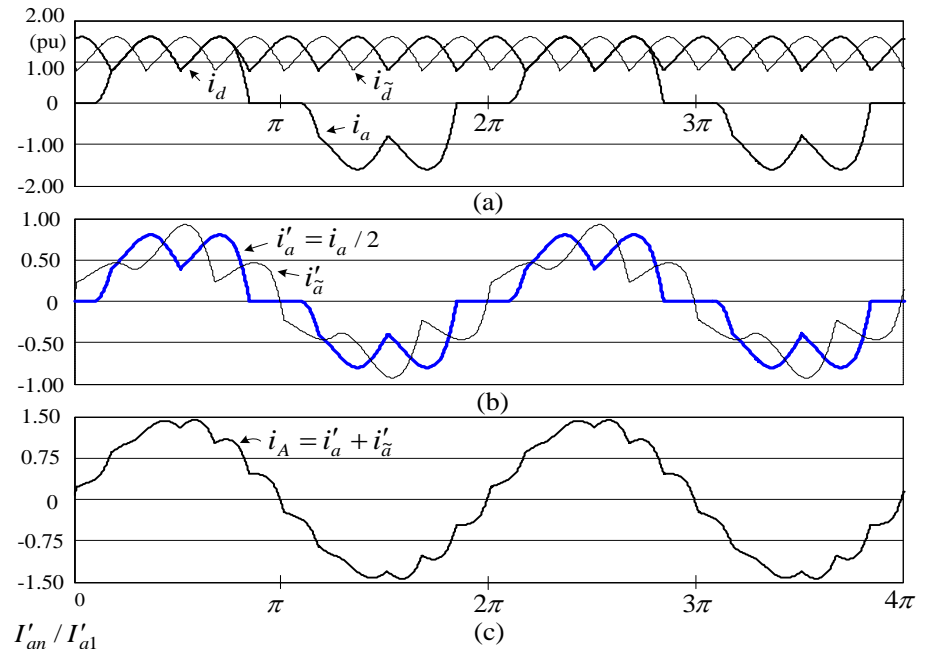


- Comparison with series-type:

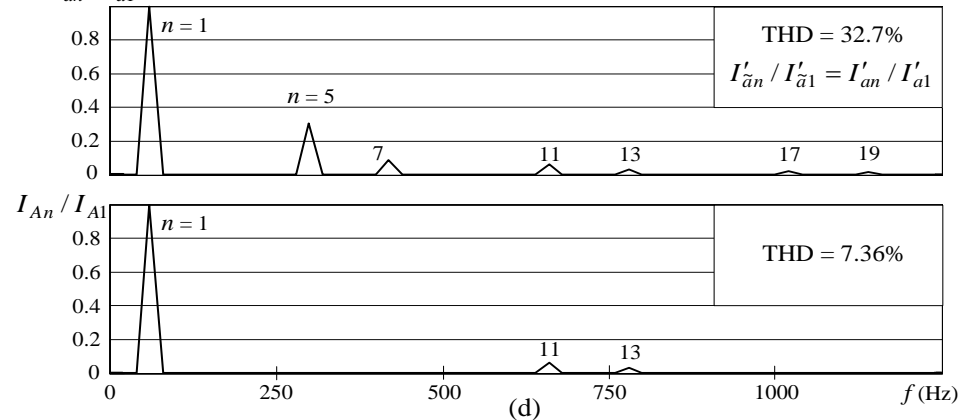- DC current ripple: higher
- Line current THD: close




# 24-pulse Diode Rectifier

- Measured Waveforms

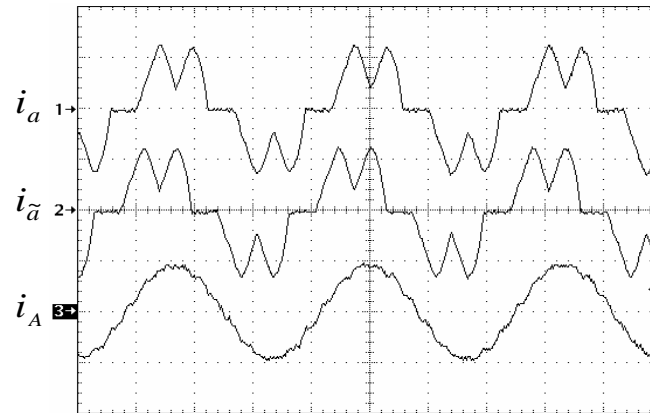

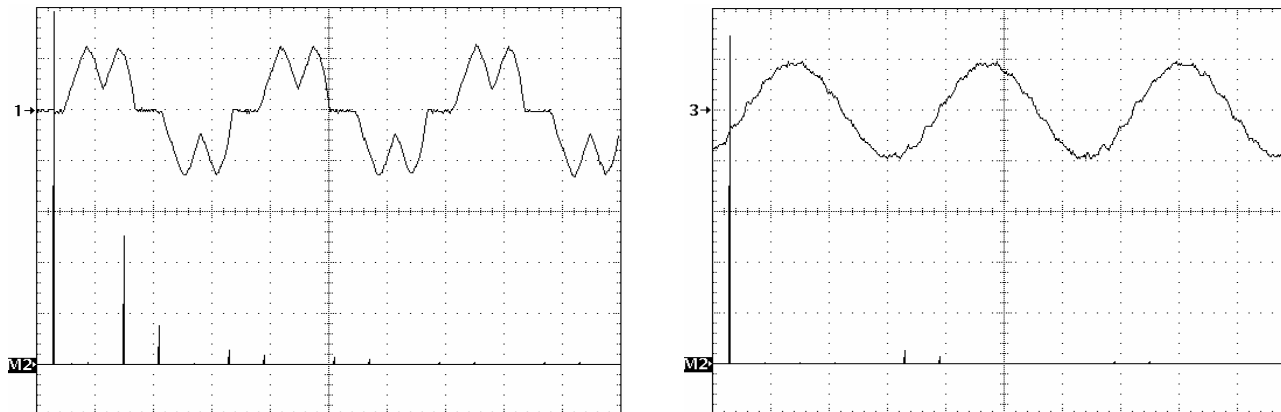
(a) Currents:  $\sqrt{2}$  pu/div, 5ms/div



(b) Spectrum:  $\sqrt{2}/10$  pu/div, 200Hz/div

# 12-pulse Diode Rectifier (separate Type)

- Rectifier Topology

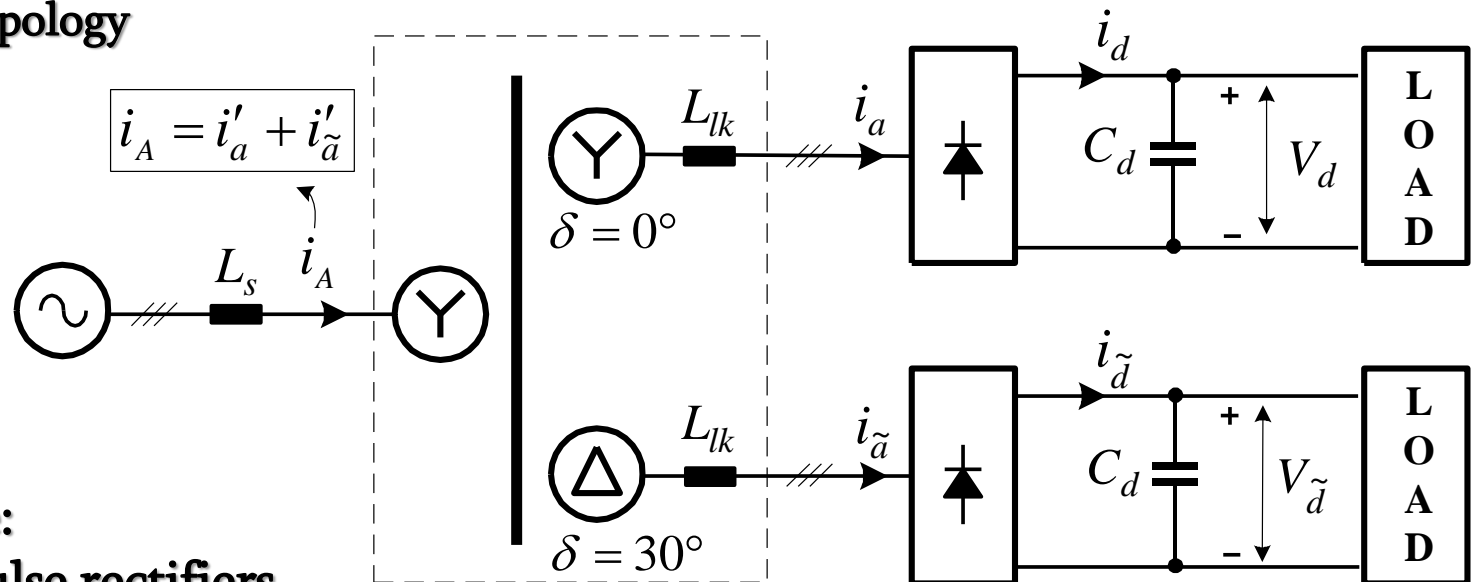

- Series type:  
Two six-pulse rectifiers are in Parallel at the output.

- Phase shifting transformer:

$$\delta = \angle V_{\tilde{a}\tilde{b}} - \angle V_{AB} = 30^\circ$$

- Secondary line-to-line voltage:


$$V_{ab} = V_{\tilde{a}\tilde{b}} = V_{AB} / 2$$

- Turns ratio:  $\frac{N_1}{N_2} = 2$  and  $\frac{N_1}{N_3} = \frac{2}{\sqrt{3}}$ .




# 12-pulse Diode Rectifier (separate Type)

## • Typical Waveforms

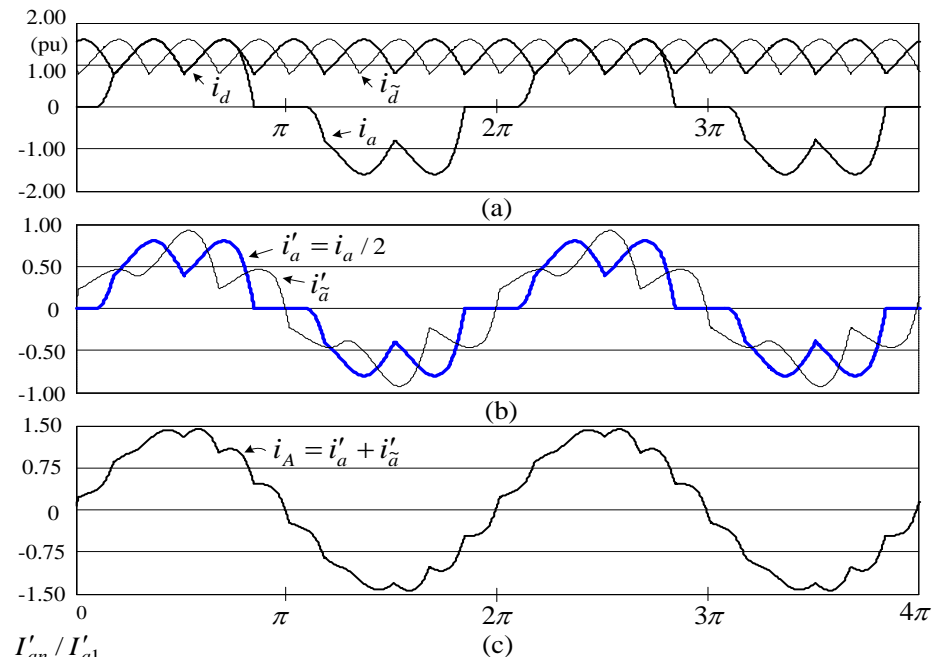


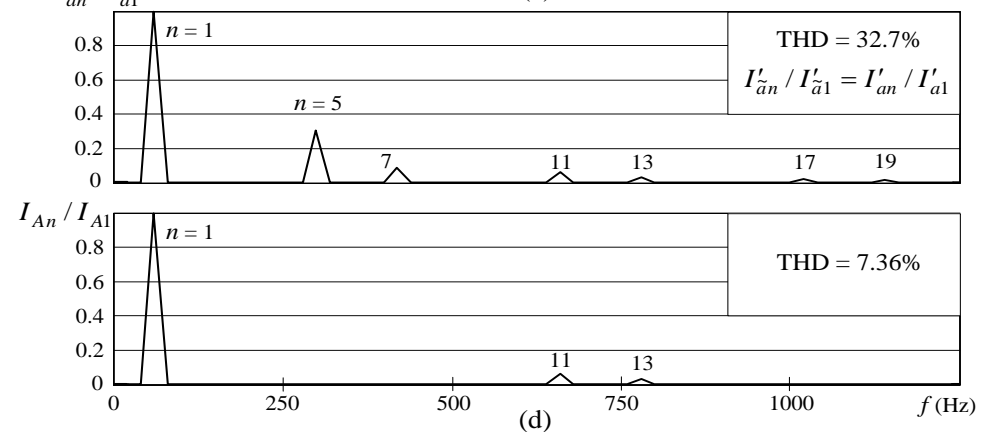- Comparison with series-type:
  - DC current ripple: higher
  - Line current THD: close




# 12-pulse Diode Rectifier (separate Type)

- Measured Waveforms

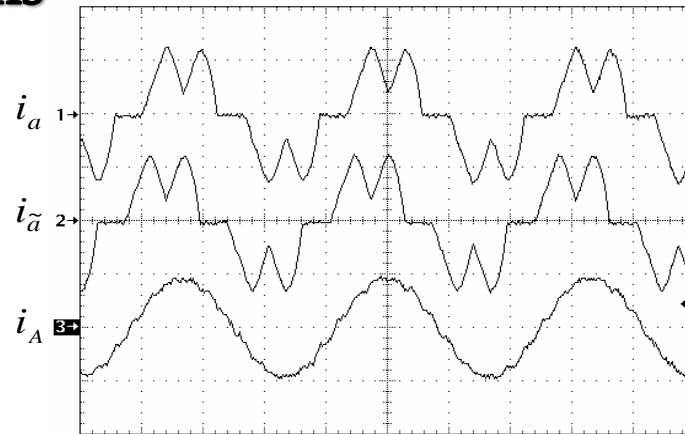

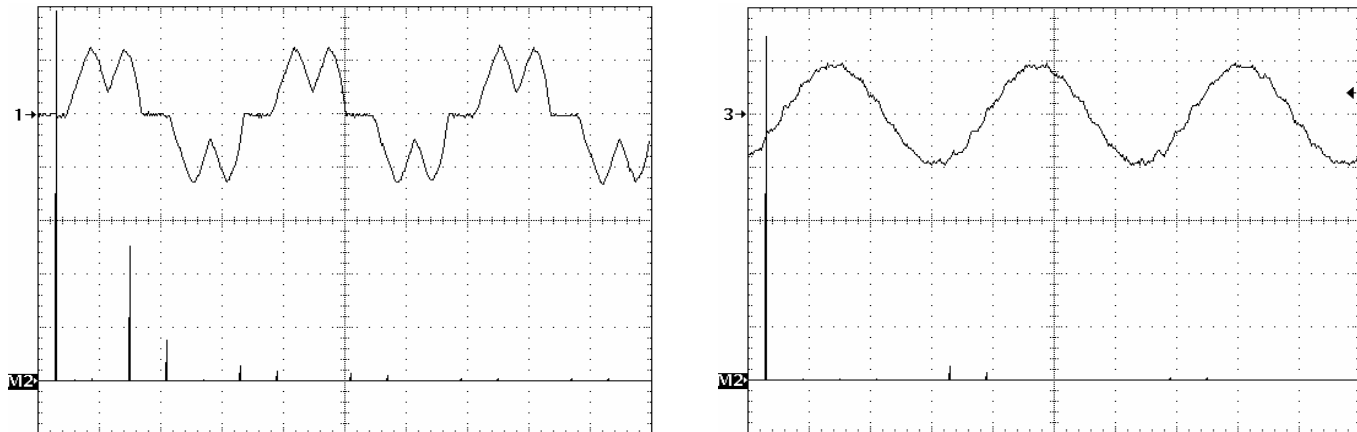
(a) Currents:  $\sqrt{2}$  pu/div, 5ms/div



(b) Spectrum:  $\sqrt{2} / 10$  pu/div, 200Hz/div


# 18-pulse Diode Rectifier

- Rectifier Topology

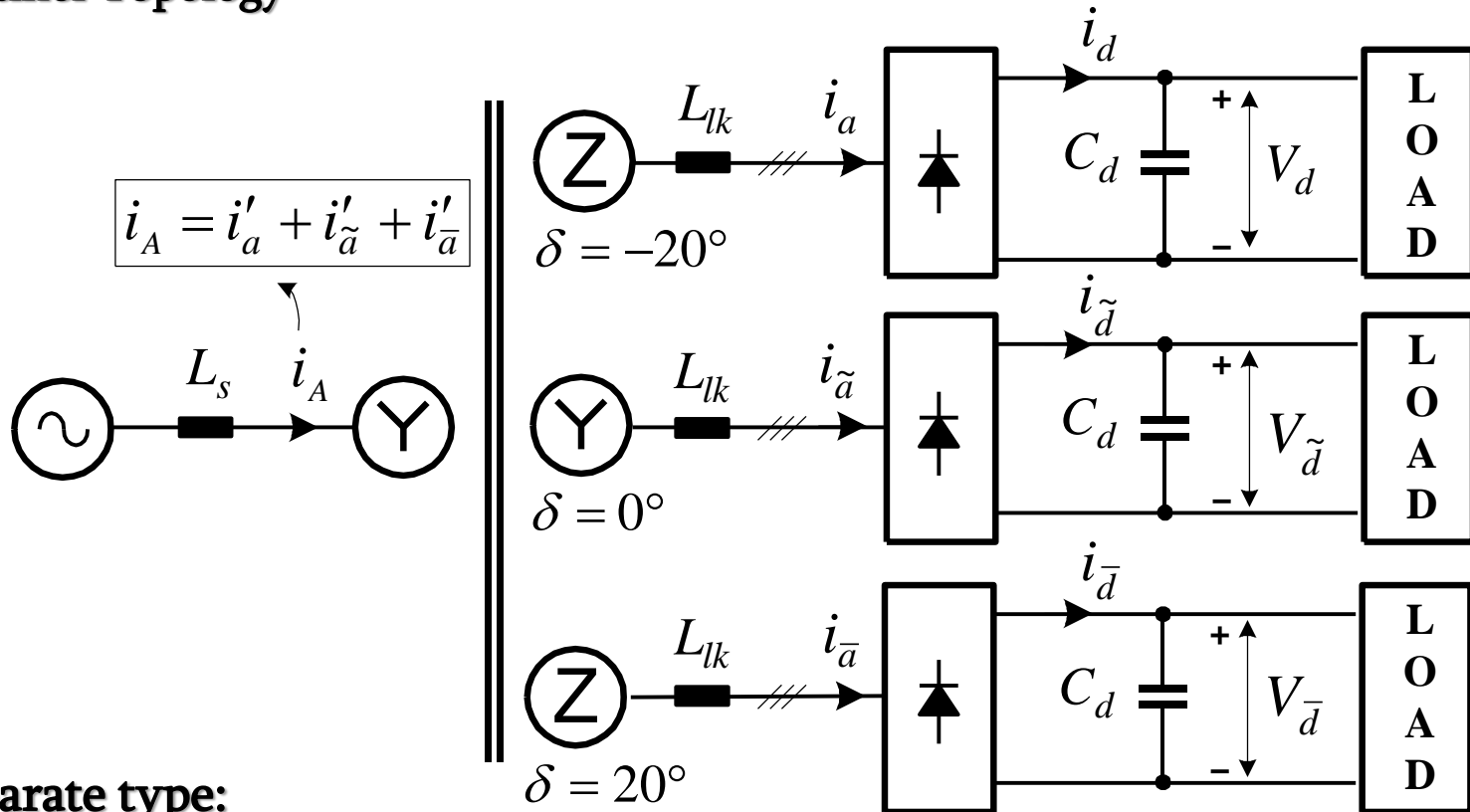

- Separate type:  
Three six-pulse rectifiers  
are in parallel at the output.

# Application Example

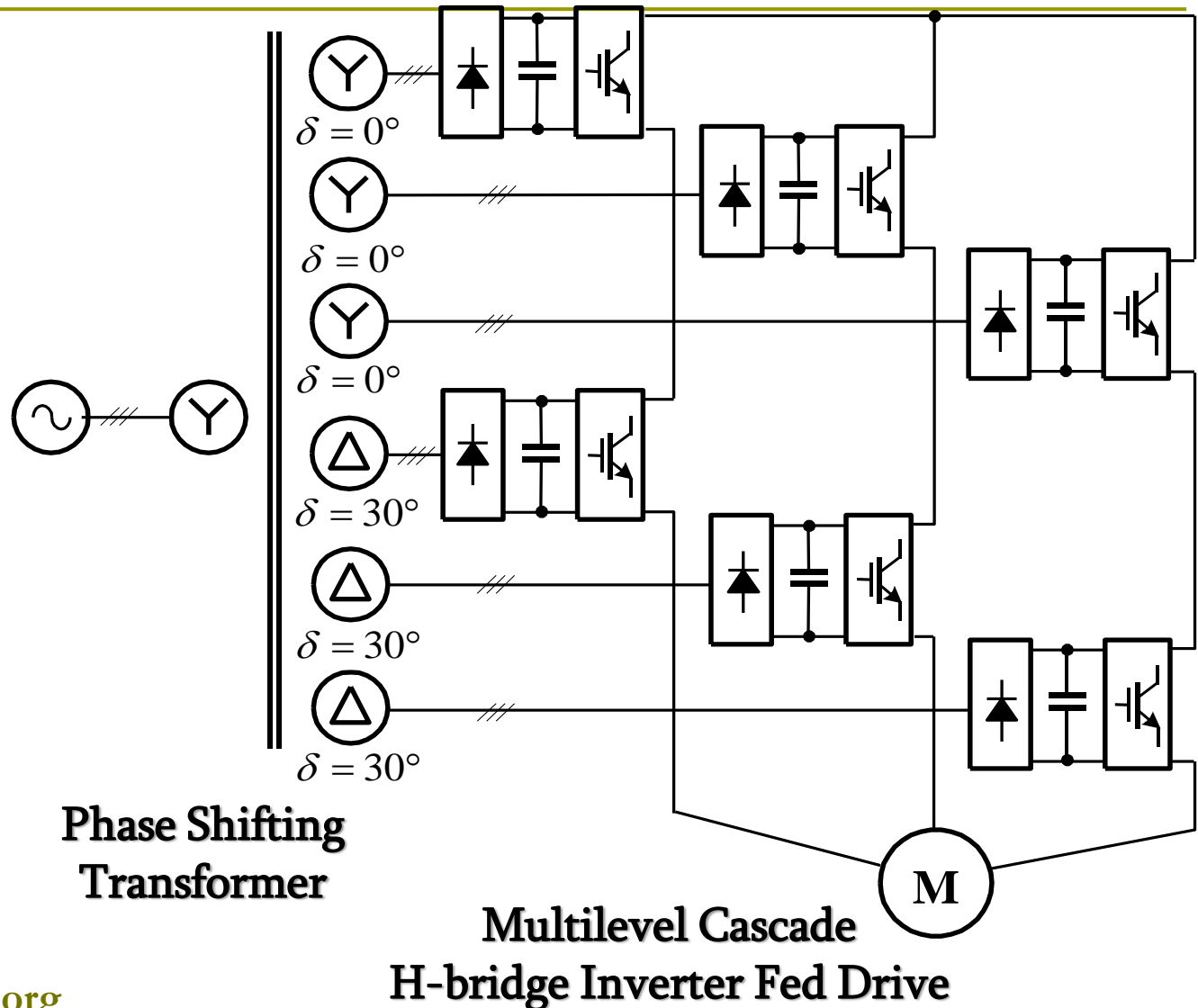

# Reference

---

• **Book:**

**High power converters and AC drives, Bin Wu**

# Thank

---

# You

[www.vishaldevdhar.org](http://www.vishaldevdhar.org)