

# Chapter-4 Power supplies

## Switched Mode Power Supply

↳ Linear DC power supply operates on active region of the semiconductor device which increases on state power loss.

↳ Also in other power supplies based on phase-controlled rectifier needs large filter to reduce voltage ripple in the DC output voltage.

↳ This large filter makes the design of the power supply bulky.

↳ SMPS works on chopper, by operating the ON/OFF switch rapidly, as ac ripple frequency rises which can be easily filtered by L & C filter which are very small in size & weight.

↳ SMPS is based on chopper principle


## Advantages of SMPS

- ↳ Isolation between the source & load
- ↳ High power density for reduction of size & weight
- ↳ Controlled direction of power flow
- ↳ High conversion efficiency.
- ↳ Input & output waveforms with a low THD for small filters.
- ↳ Controlled power factor if the source is an ac voltage.

## Different Topologies of SMPS (Isolated)

- ↳ Flyback converter (Buck-Boost)
- ↳ Forward converter (Buck)
- ↳ Push-pull converter (Buck)
- ↳ Half bridge converter (Buck)
- ↳ Full bridge converter (Buck)
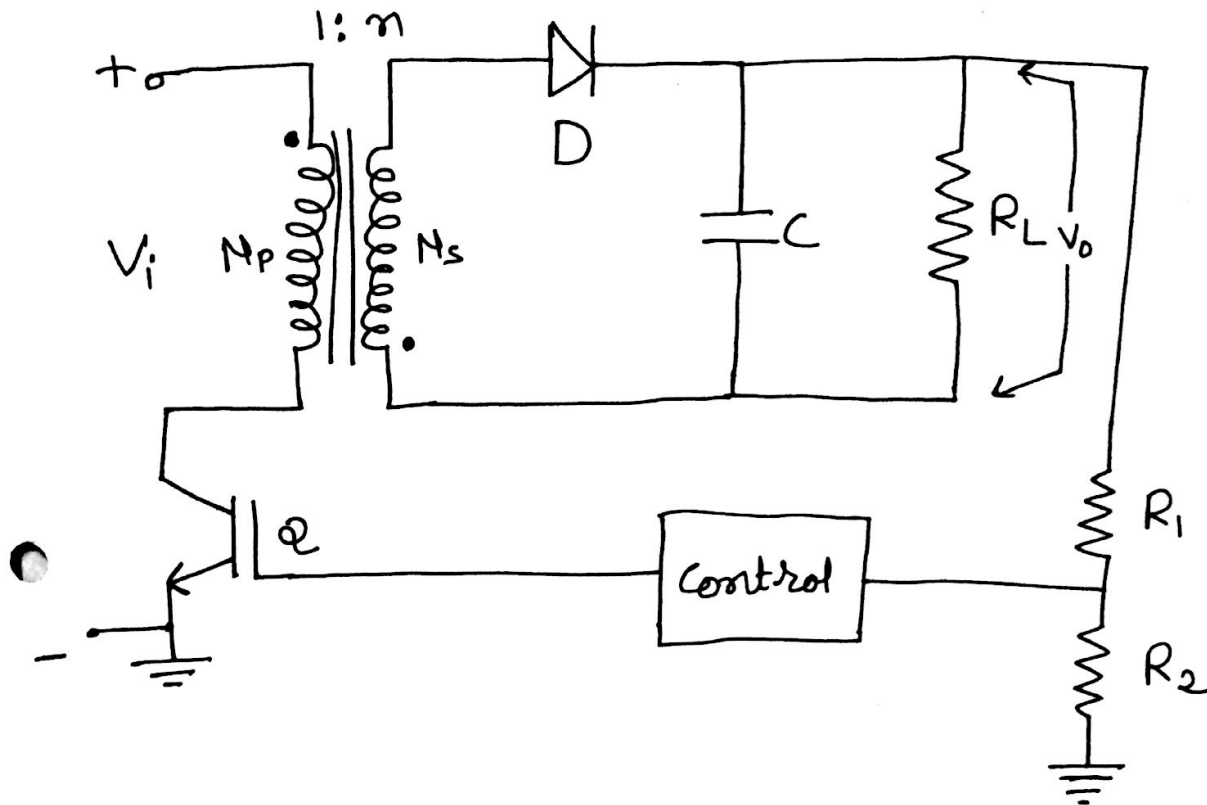
# Flyback Converter (Buck-Boost Based Isolated) Converter



- ↳ Flyback converter is most popular converter
- ↳ This converter has very least component count.
- ↳ This works on buck-boost converter topology.
- ↳ The dot polarities on winding is introduced to measure the o/p voltage in the conventional positive sense.
- ↳ There are two switches  $Q$  &  $D$ , both are operated out of phase, observed by dot polarities of two winding inductor.
- ↳ Two winding inductor (Xformer) provides isolation between source & load.

There are two operating modes of the converter.

Mode-I Q is ON

↳ When switch Q is ON the inductor energy builds up for the period  $kT$ .

Where  $k \equiv \text{duty cycle} = \frac{T_{\text{ON}}}{T}$   
 $T \equiv \text{Total time}$

$$T_{\text{ON}} = T - T_{\text{OFF}}$$

$$\underline{T_{\text{ON}} = kT}$$

$$T_{\text{OFF}} = T - T_{\text{ON}}$$


$$= T - kT$$

$$\underline{T_{\text{OFF}} = (1-k)T}$$

↳ During this mode inductor energy builds up as it now directly connected to source  $V_i$ .

↳ During this time output voltage is supplied by capacitor C by discharging it through load.

↳ Diode D is reversed biased.

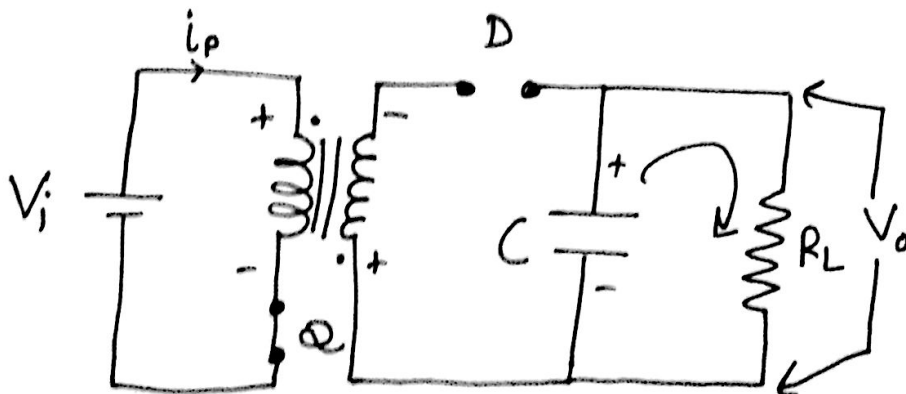

$$\hookrightarrow V_1 = V_i$$

$$V_2 = -\cancel{V_i} = V_i n$$

$\hookrightarrow$  There is no energy transferred from IP to load.

$$\hookrightarrow i_p = \frac{V_i t}{L_p}$$

$L_p =$  Magnetizing inductance


$t = kT \rightarrow$  at the end

Peak Primary current

$$\hookrightarrow I_p = \frac{V_i kT}{L_p}$$


Peak Secondary current

$$I_s = \frac{I_p}{n}$$

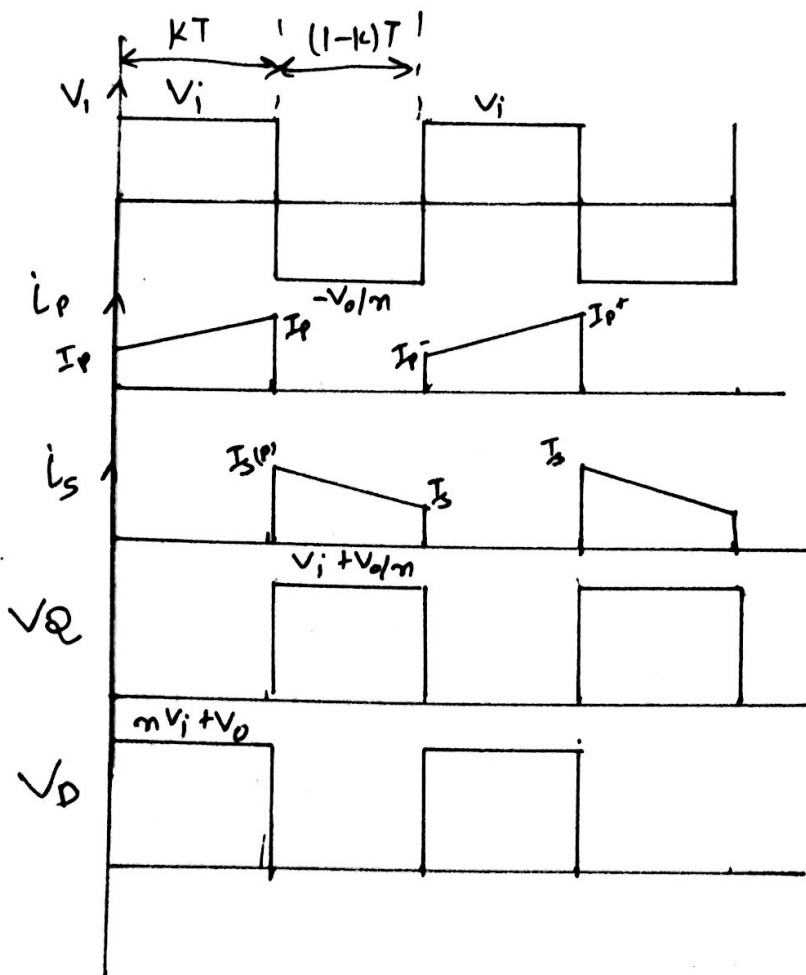
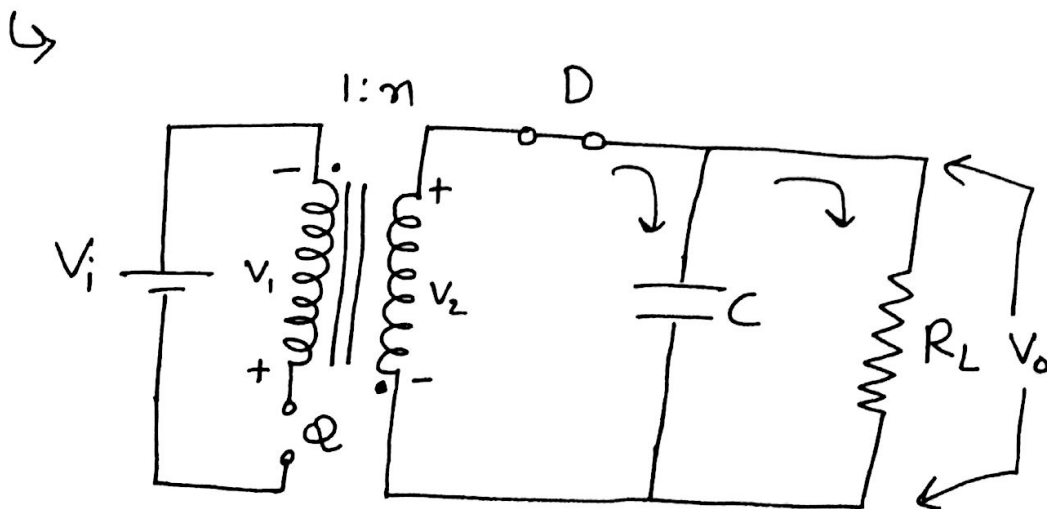
## Mode-II Q is OFF

- ↳ During this time switch Q is off.
- ↳ Due the reverse polarity Diode D is now forward biased
- ↳ The non dot end becomes positive
- ↳ The primary winding of inductor is now out of action.
- ↳ The secondary winding now discharges the energy stored in the core to the capacitor and load.



$$\hookrightarrow V_2 = -V_o = -\frac{V_i}{n}$$

$$\hookrightarrow i_s = I_s - \frac{V_o t}{L_s}$$

$L_s$  = Magnetizing inductance of secondary

- ↳ During  $kT$  period switch  $Q$  is ON and the voltage across the primary is  $V_i$ .
  - ↳ The current through primary is  $i_p$ .
  - ↳ Voltage across secondary is  $nV_i$ .
  - ↳ The voltage across  $D$  is  $nV_i + V_o$ .
- ↳ During  $(1-k)T$  period  $D$  is conducting.
    - ↳ Voltage across the secondary is  $V_o$ .
    - ↳ Voltage across the primary is  $\frac{V_o}{n}$ .
    - ↳ Voltage across  $Q$  is  $V_i + \frac{V_o}{n}$ .

### Output voltage

$$V_i T_{ON} = \frac{V_o}{n} T_{OFF}$$

$$V_o = nV_i \frac{T_{ON}}{T_{OFF}}$$

$$= nV_i \frac{kT}{(1-k)T}$$


$$V_o = nV_i \left( \frac{k}{1-k} \right)$$

## Buck Based Isolated Converter


- ↳ Forward converter
- ↳ Push-pull converter
- ↳ Half-Bridge converter
- ↳ Full Bridge converter
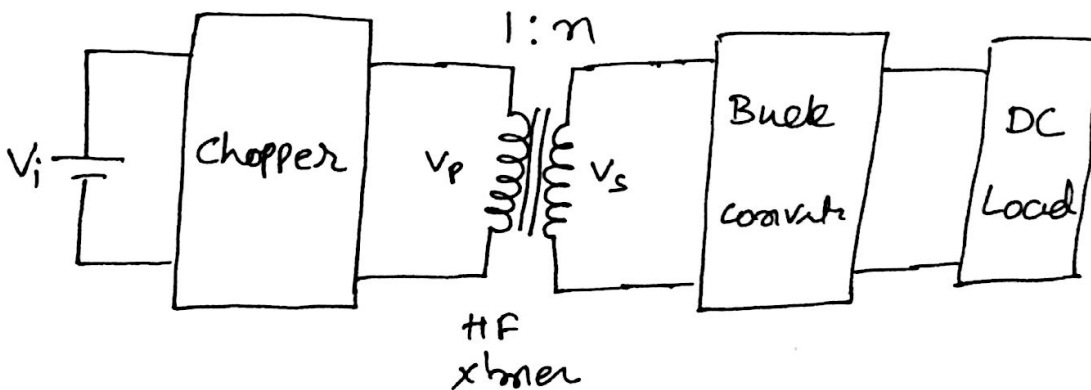
### ↳ Forward Converter


↳ Power flow is from the input source to the output through the transformer in only in one direction. the converter is called forward converter.






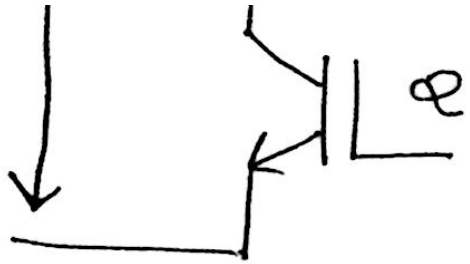


During Time  $\frac{KT}{\phi}$  is ON

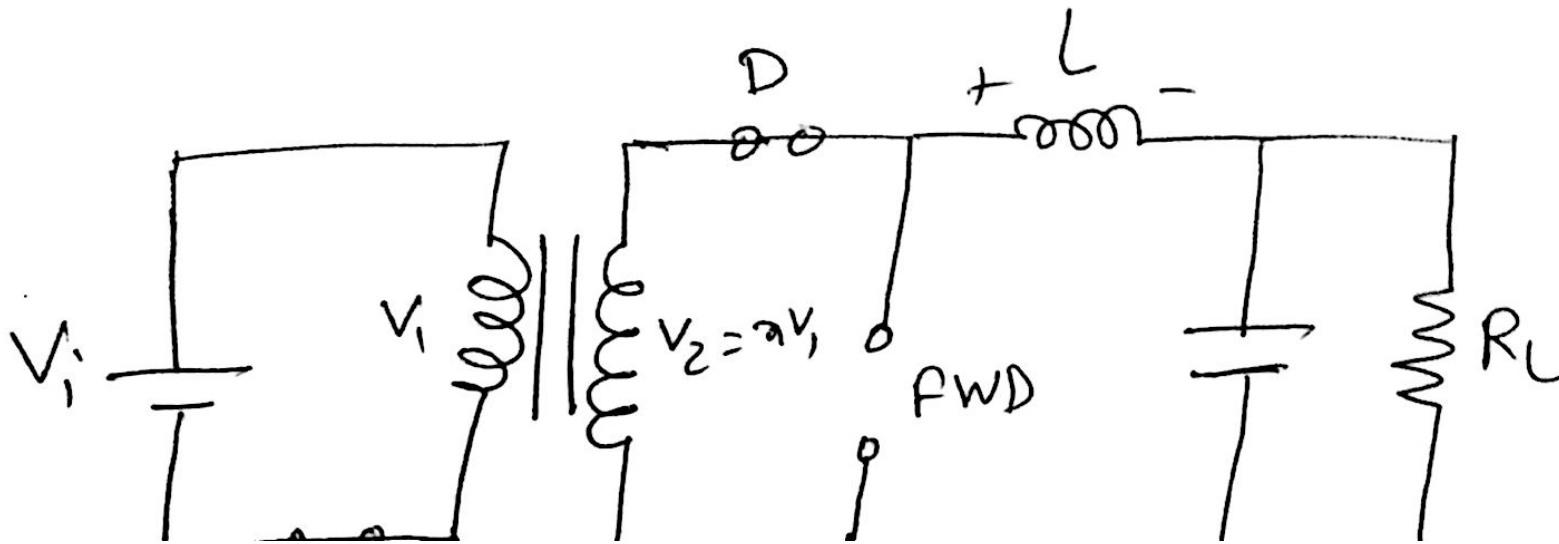


During Time  $(1-k)T$  Q-OFF

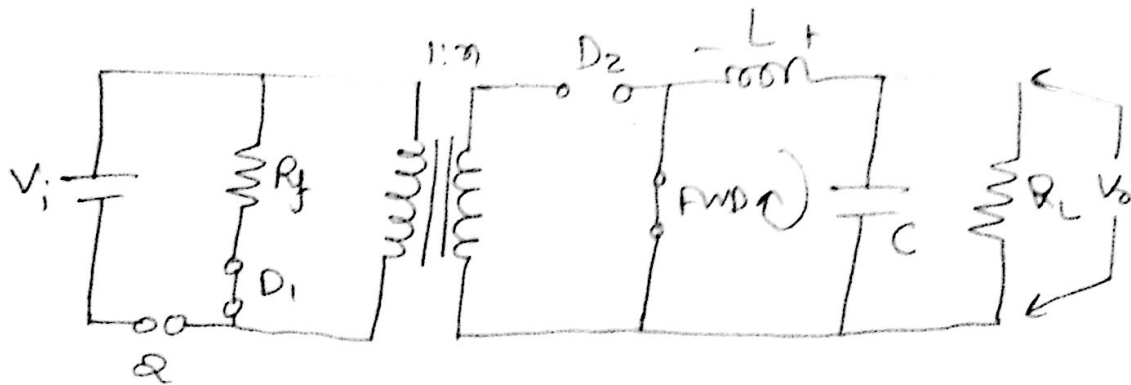

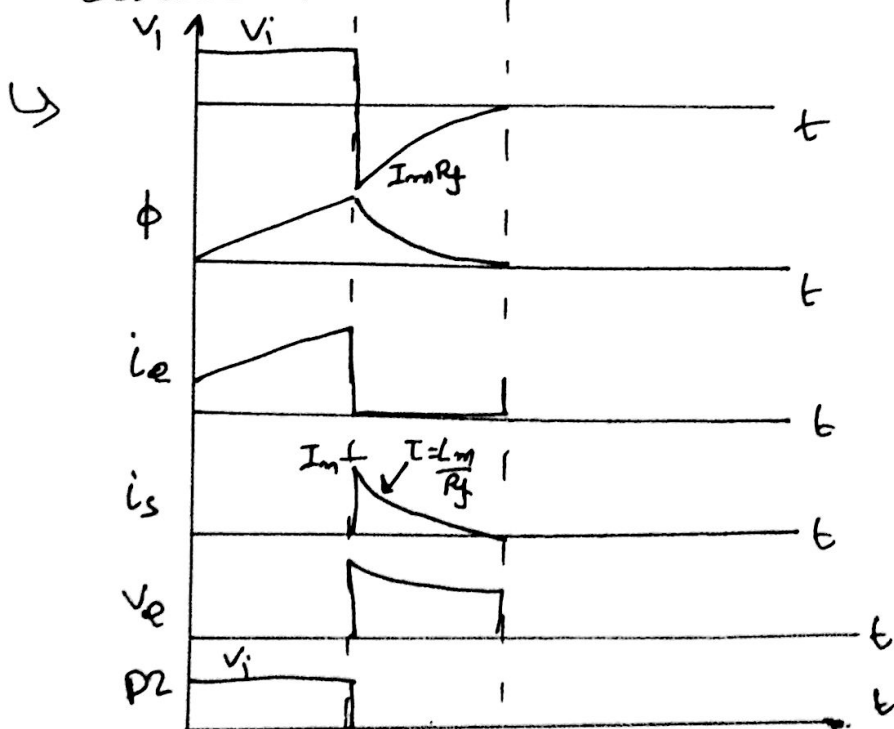- ↳ During time  $(1-k)T$  switch is closed open
- ↳ No current is flowing through the secondary of transformer
- ↳ Primary current is interrupted.
- ↳ Sudden cut off of primary current implies a negative  $di/dt$  and therefore voltage across primary is reversed.


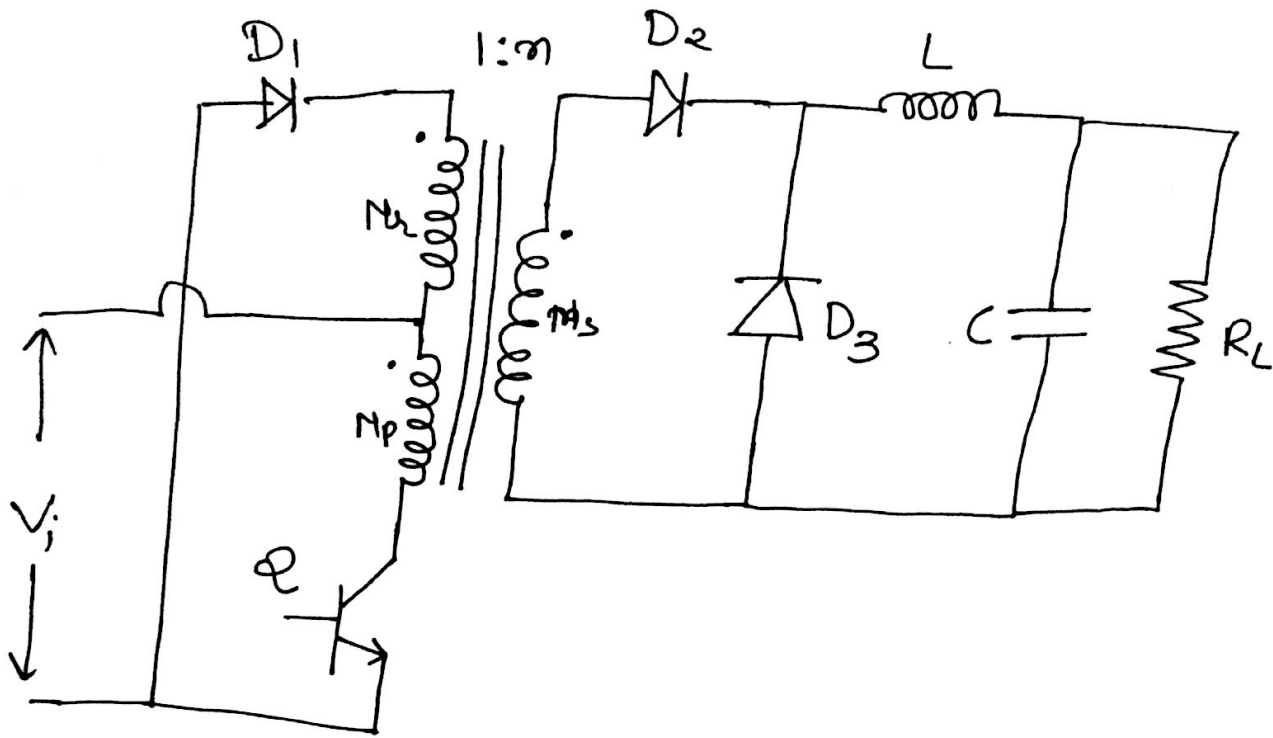
## Forward converter (Demagnetizing winding)



- ↳ Here there are three windings used in transformer.
- ↳ The transformer core is reset by reset winding (Demagnetizing winding)
- ↳ The energy stored in the transformer core is returned to the supply and the efficiency is increased.
- ↳ The dot on the secondary winding is so arranged that output diode  $D_2$  is forward biased when the voltage across primary is positive. When  $Q$  is on.

↳  $D_2$  is now forward biased due to positive voltage across secondary.

↳ The capacitor is charged and  $v = nV_1$  voltage appears across load.

↳ As  $D_1$  is reversed biased no ~~net~~ current flowing in the demagnetizing winding.

### Mode-II $(1-k)T$

↳ During time  $(1-k)T$  the switch  $Q$  is off and  $D_f$  is ON.

↳ The primary current is cut-off suddenly when  $Q$  is off.

↳ This makes a negative  $di/dt$  that will reverse the primary voltage polarity making the non-dot end positive.

↳ Non-dot end of demagnetizing winding +ve.

↳ This will cause the current to flow thro' the demagnetizing winding against the  $V_1$ .


↳ The voltage across the demagnetizing winding will be  $V_1$  which will cause the flux in the core to decay linearly.

↳ If  $N_2 = N_1$  then for the flux that built up to maximum of  $\phi_m$  during  $DT$  will decay to zero in exactly the same time when  $Q$  is OFF &  $D_2$  is ON.

↳  $N_2 = N_1$ ,  $(1-k)T > kT$  to insure flux will decay to zero.

↳ It can be seen that  $k < 0.5$ .

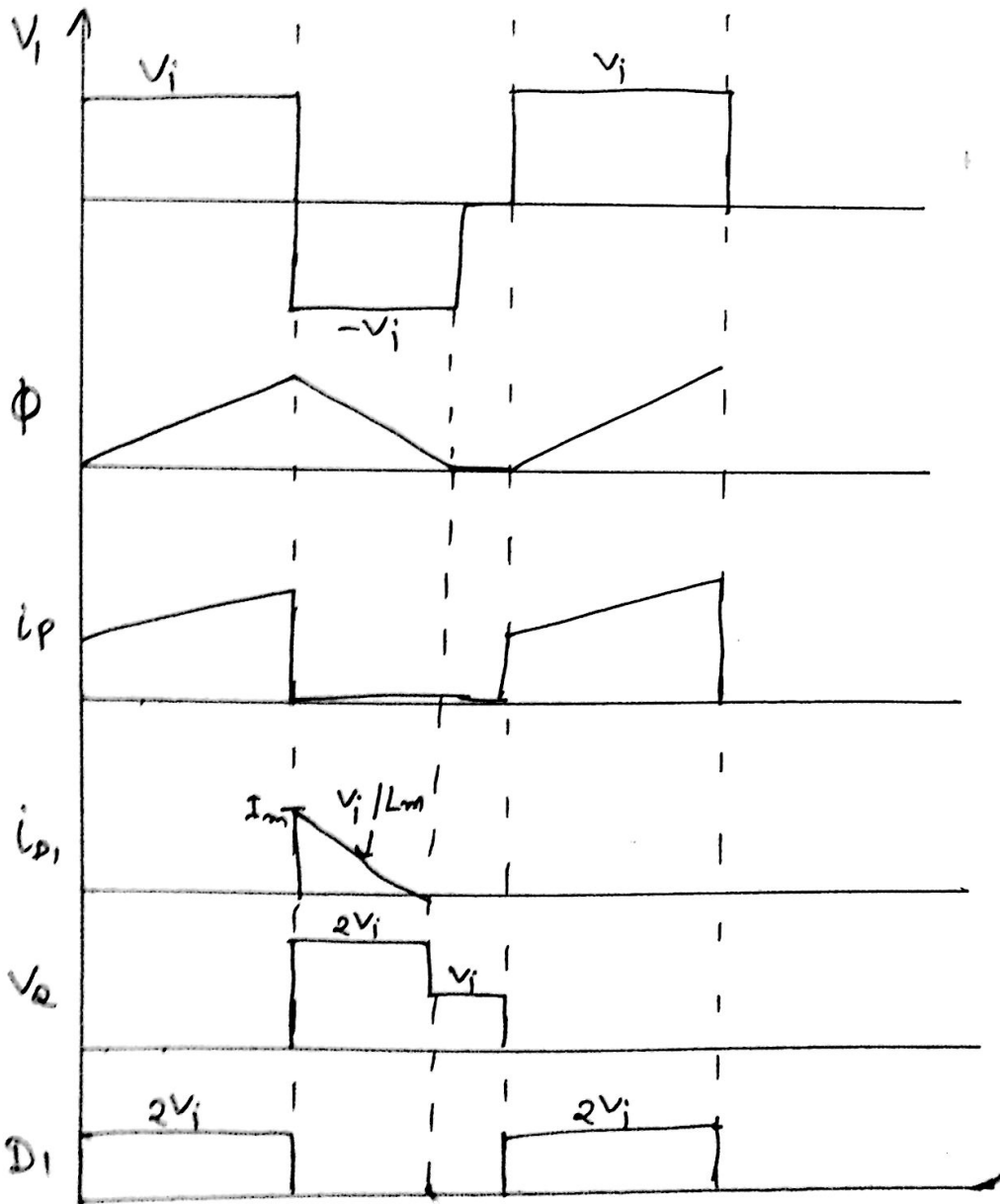i.e. maximum duty cycle is limited to 0.5.



# Push-Pull Converter


↳ Forward converter utilizes only the positive half of the core magnetization as the magnetizing current & the core flux are unidirectional.

• ↳ Therefore the core is under utilized and core size for given power output is large than if it is utilized in both directions.


↳ The push-pull converter magnetize the core in both directions to better utilize the core.

• ↳ In push-pull converter two forward converters are operating in back to back, hence it is named push-pull converter.

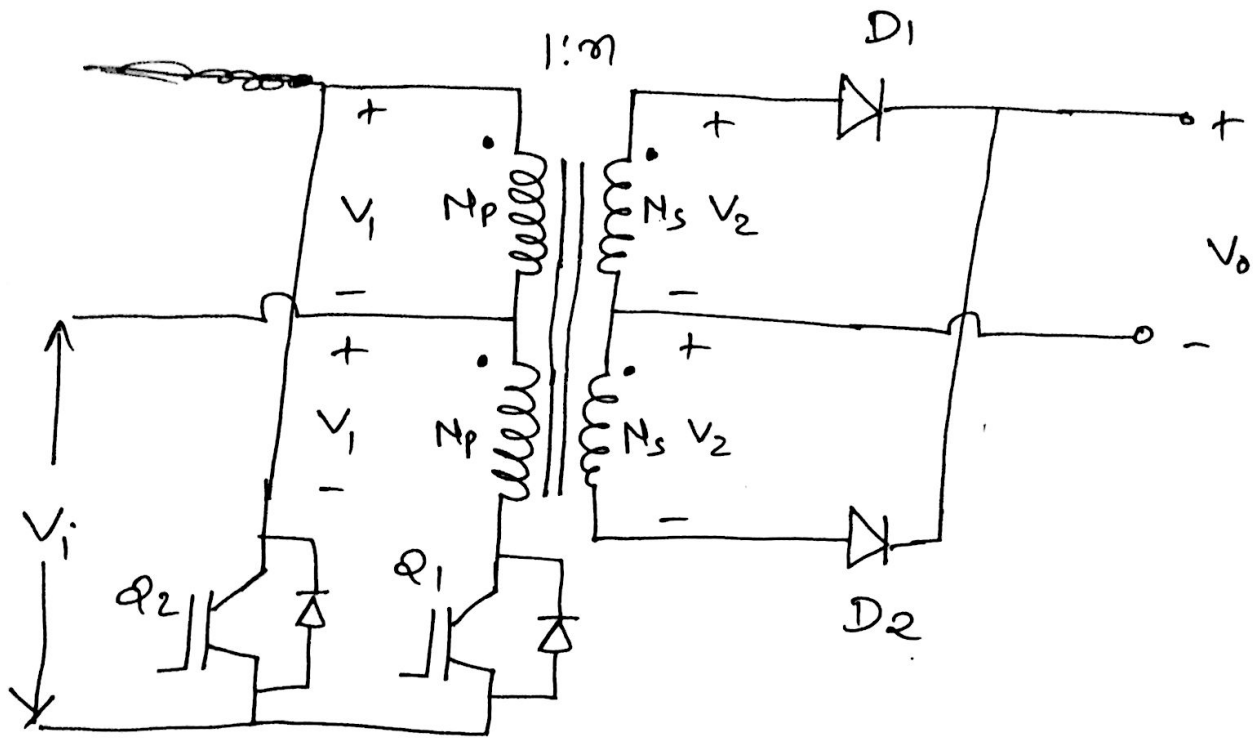
↳ During  $kT$  one forward converter is transferring power to load ; during  $(1-k)T$  another forward converter is transferring power to load.



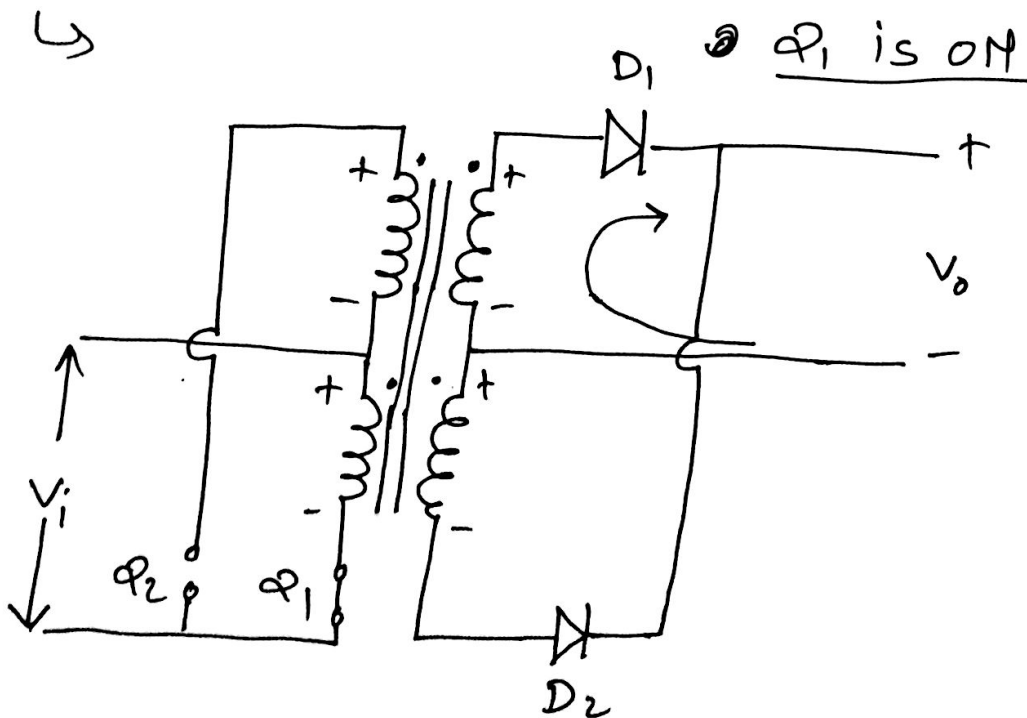
↳ Transformer is centered Tap and it consists of switch  $Q_1$  &  $Q_2$  in the primary side and di rectifying diode  $D_1$  &  $D_2$  in the secondary side.




~~C1-K)T~~ ~~Q1 & Q2 OFF~~  $Q_2$  ON

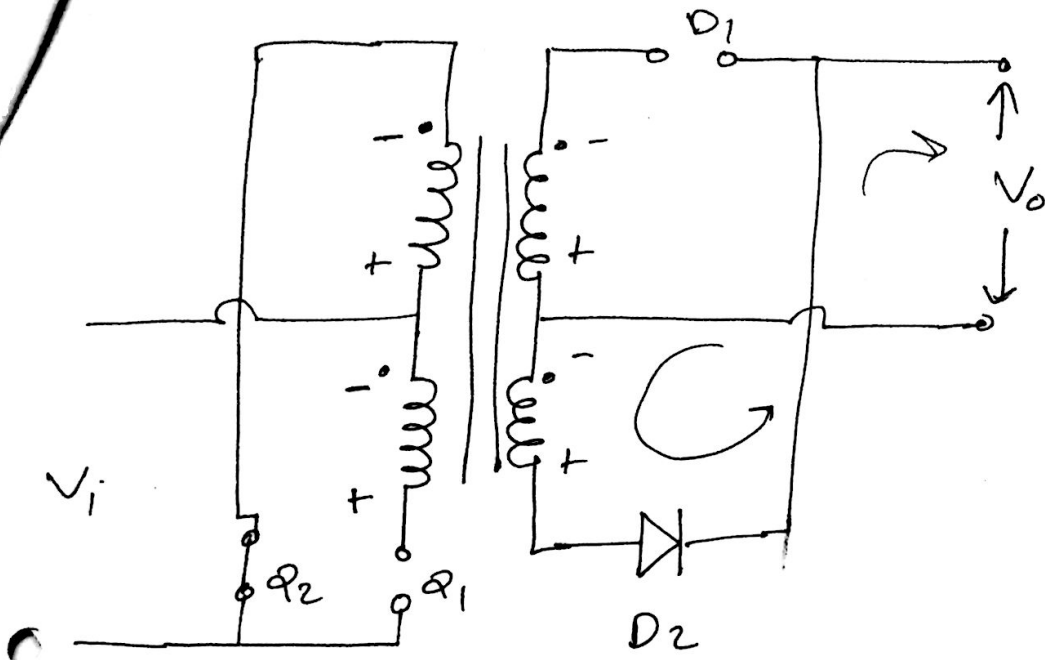



C1-K)T Period  $Q_1$  &  $Q_2$  OFF

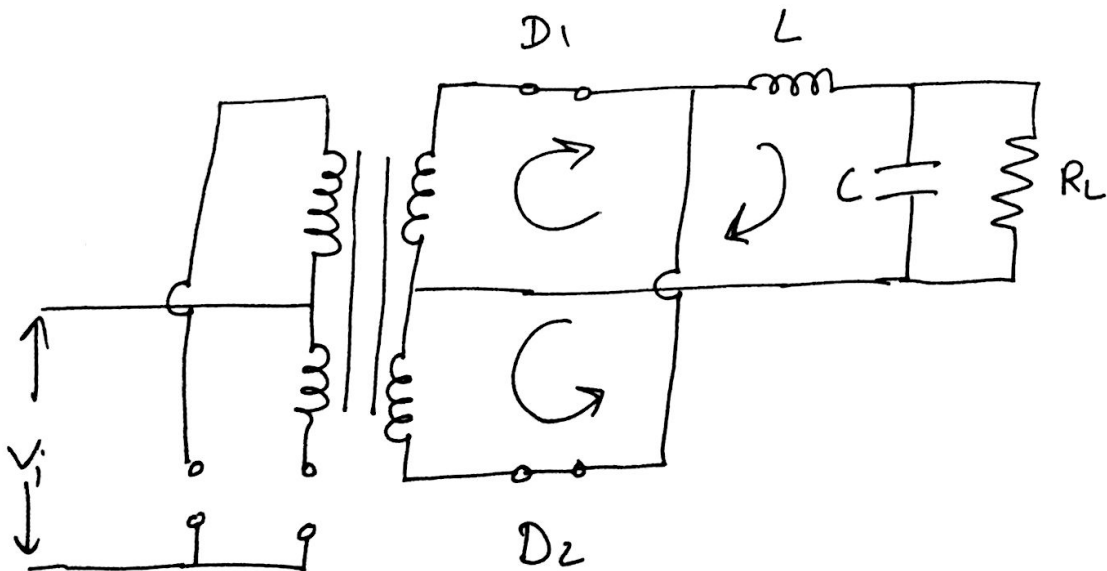





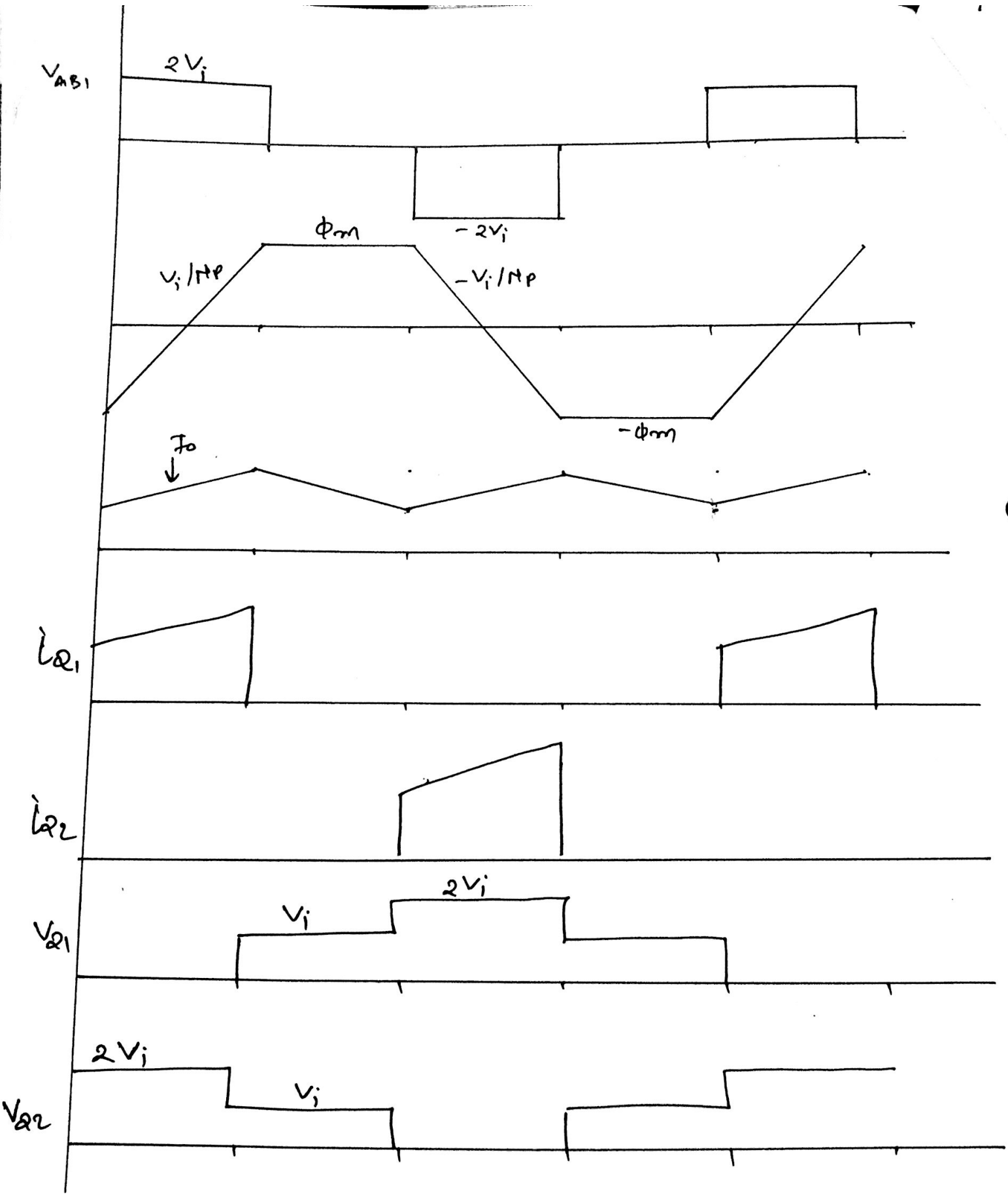

# Half Bridge Converter

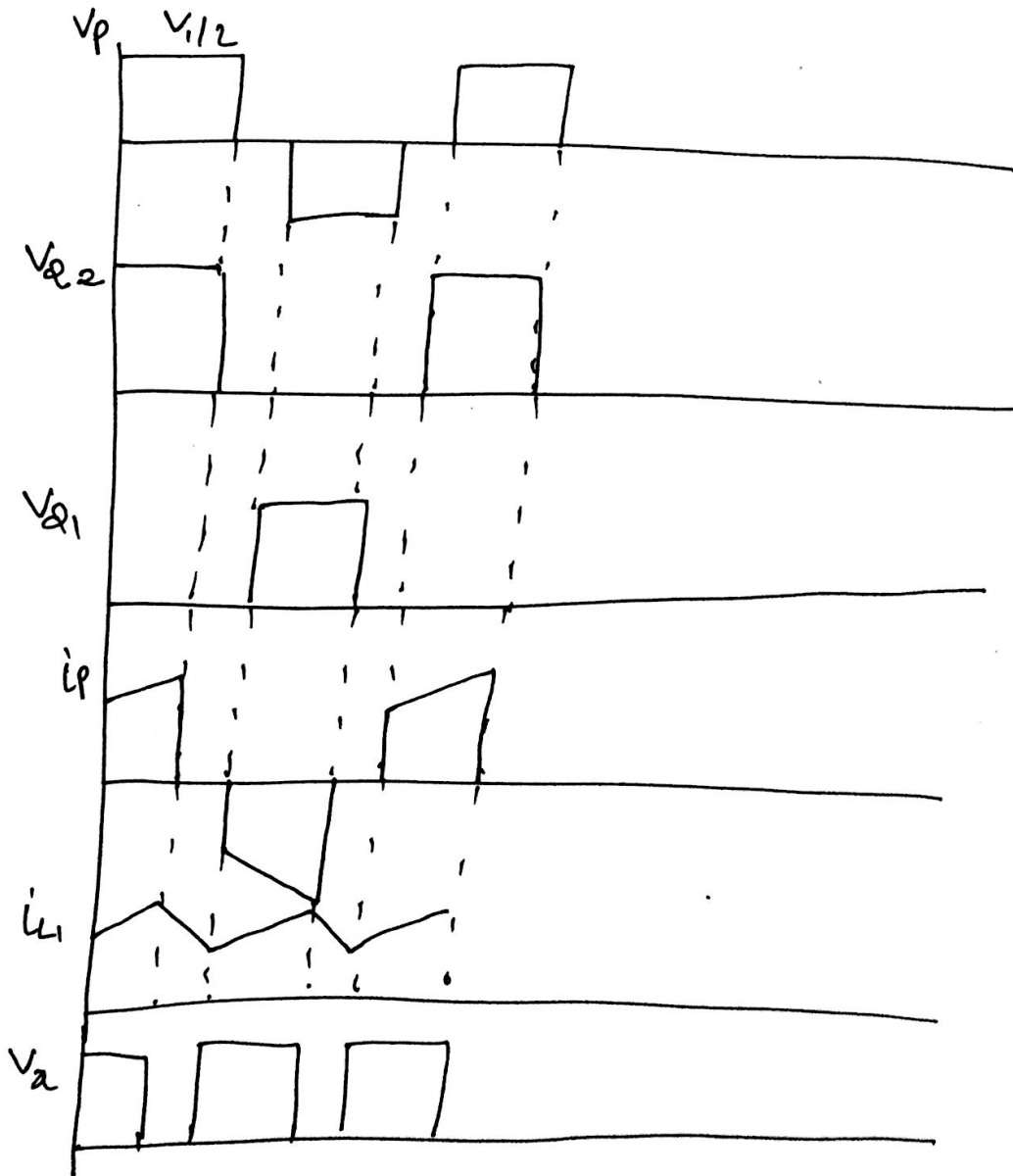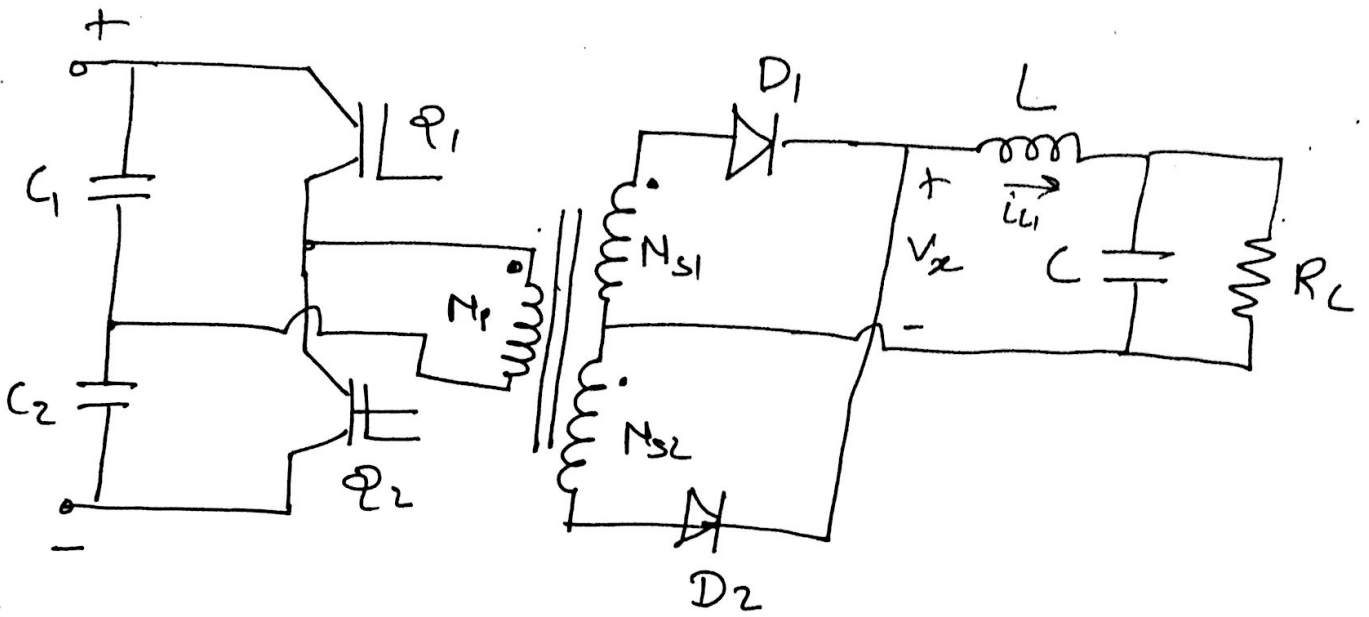


# Full Bridge Converter

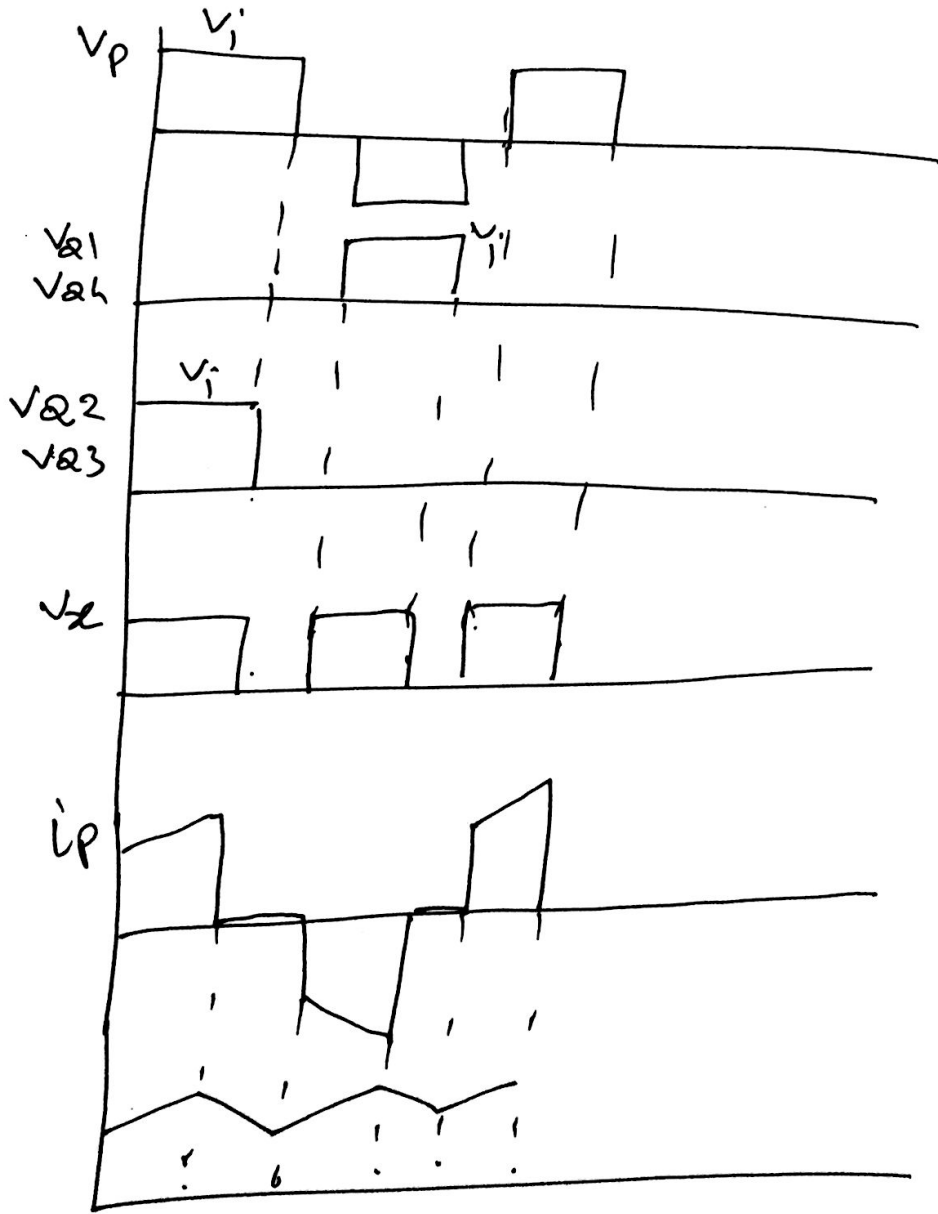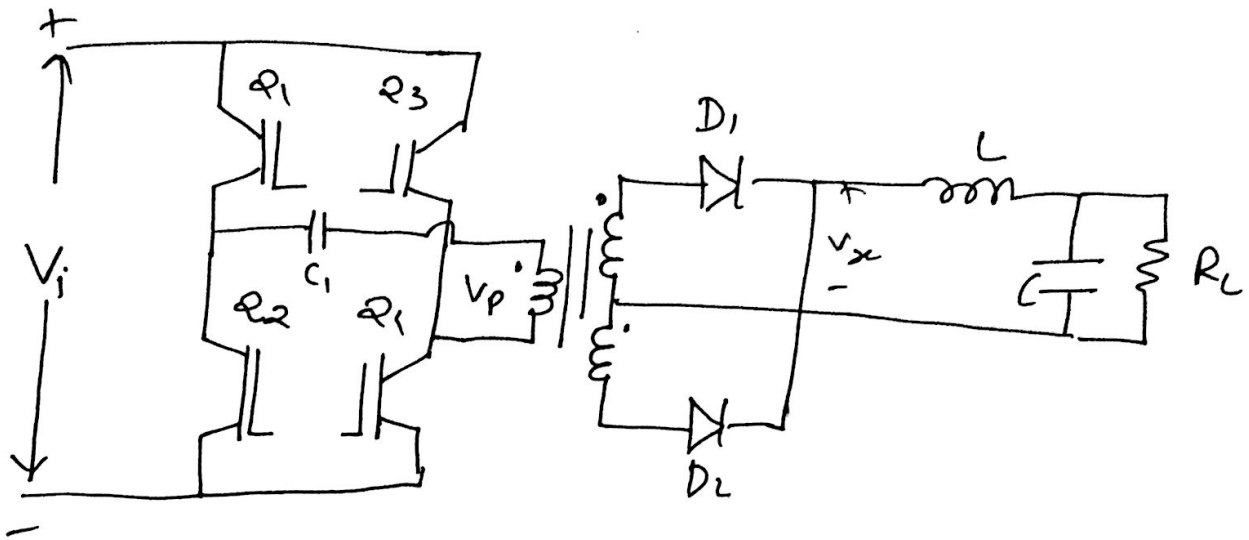

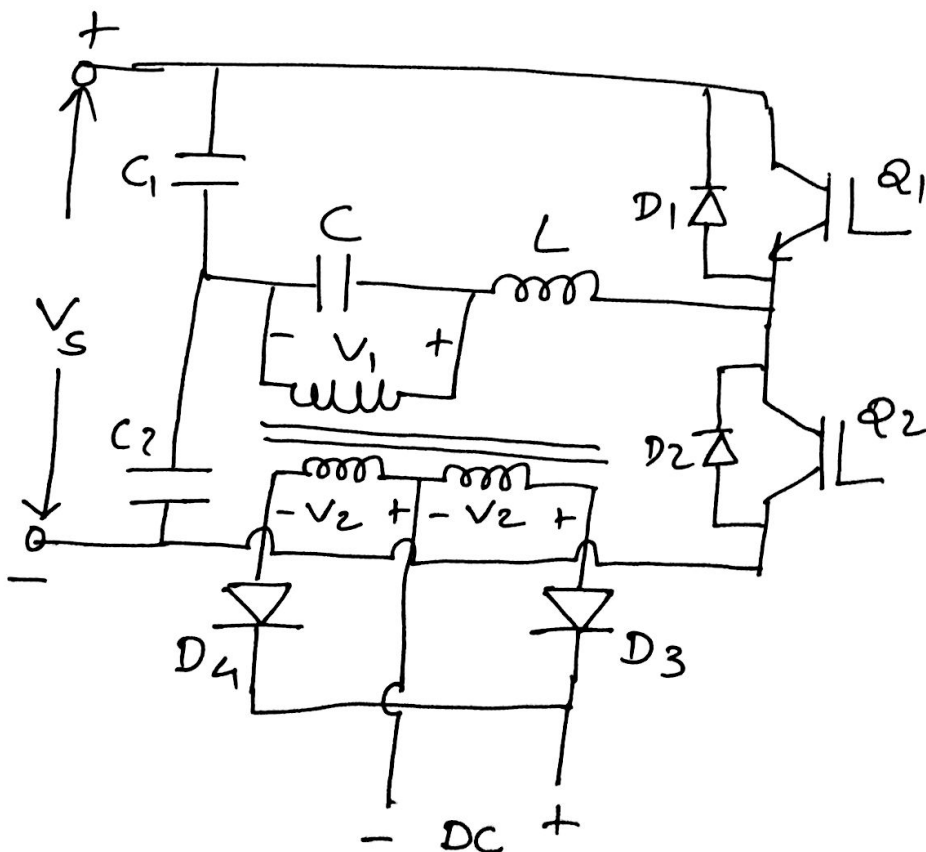
# Resonant DC Power supplies

- ↳ If the variation in DC output voltage is not wide, Resonant pulse inverter can be used.
- ↳ The inverter frequency could be same as resonant frequency.
- ↳ Inverter output voltage is sinusoidal.
- ↳ Due to resonant oscillations the  $x_{\text{turn}}$  is always reset and there are no DC saturation problems.



# Bidirectional DC Power supply

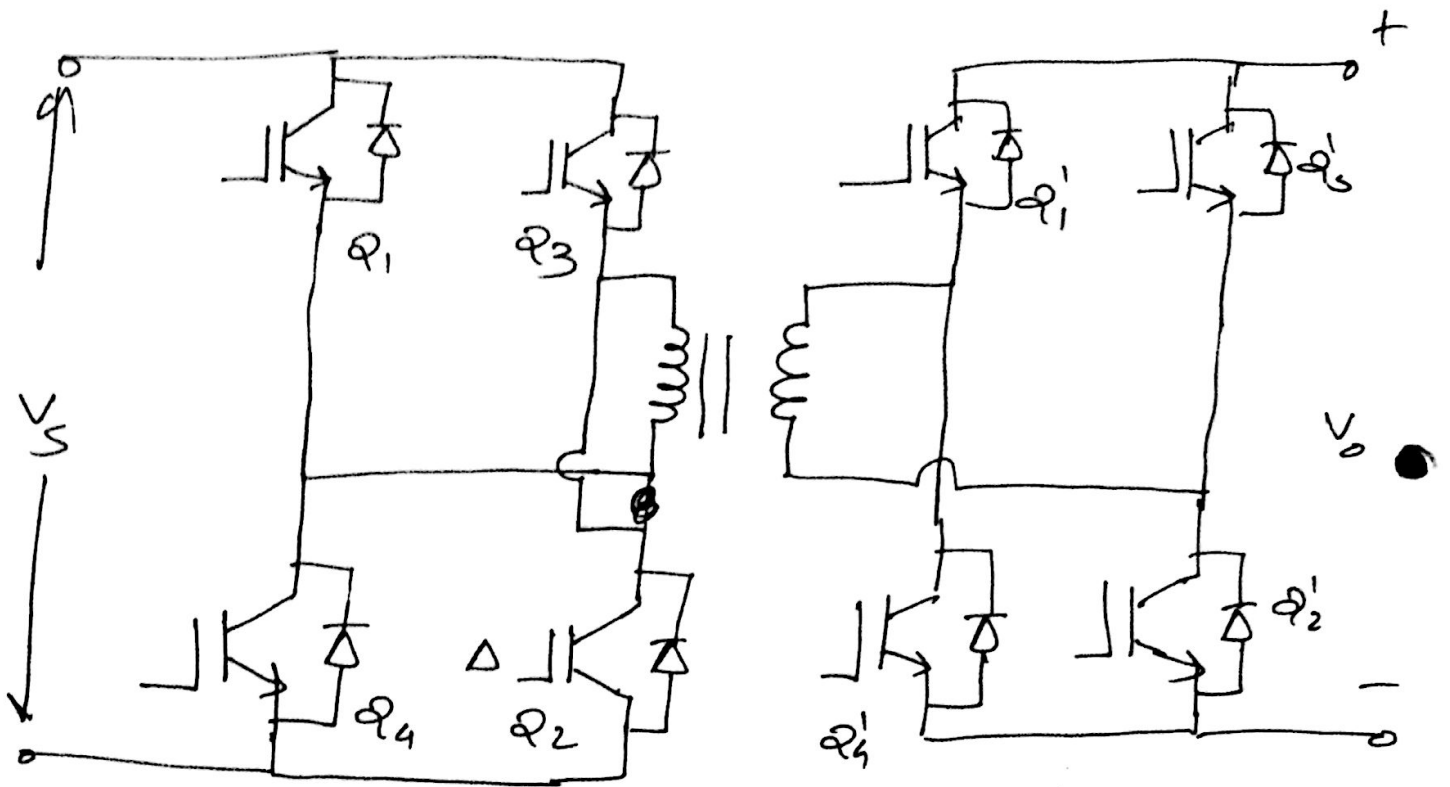

- ↳ In some applications such as Battery charger it is desirable to have bidirectional power flow capability.
- ↳ The direction of power flow depends on the values of  $V_o$ ,  $V_s$  & turns ratio  $n$ .
- ↳ If  $V_o < nV_s \Rightarrow$  source to load
- ↳ If  $V_o > nV_s \Rightarrow$  load to source

# Uninterruptible Power Supply

↳ There are some loads like

- computers
- Bio-medical instruments
- surgical equipments
- communication equipments
- Security systems
- Air Traffic controller

requires a continuous, good quality power supply.

↳ These equipments <sup>(loads)</sup> ~~requires~~ are known as critical (sophisticated) loads.

↳ These critical loads are very sensitive to the nature of power supply for their operation.

↳ These sensitive load requires a stand by power supply.

↳ These stand by power supplies are commonly known as uninterruptible power supply (UPS).

↳ UPS provides emergency power to a critical load when the utility main supply fails.

## Introduction to UPS system


- ↳ The critical load connected to a UPS is normally supplied from AC mains supply.
- ↳ When AC mains fails the critical load is transferred to an inverter which is supplied by a charged battery system.
- ↳ The inverter then takes over the mains supply.
- ↳ The transferring of load from AC mains to inverter is done by a transfer switch.
- ↳ The transfer switch is a solid state switch which usually takes 4 to 5 ms for transferring the load.

## Types of UPS

- ↳ OFF-Line UPS
- ↳ Line interactive UPS
- ↳ On-Line UPS
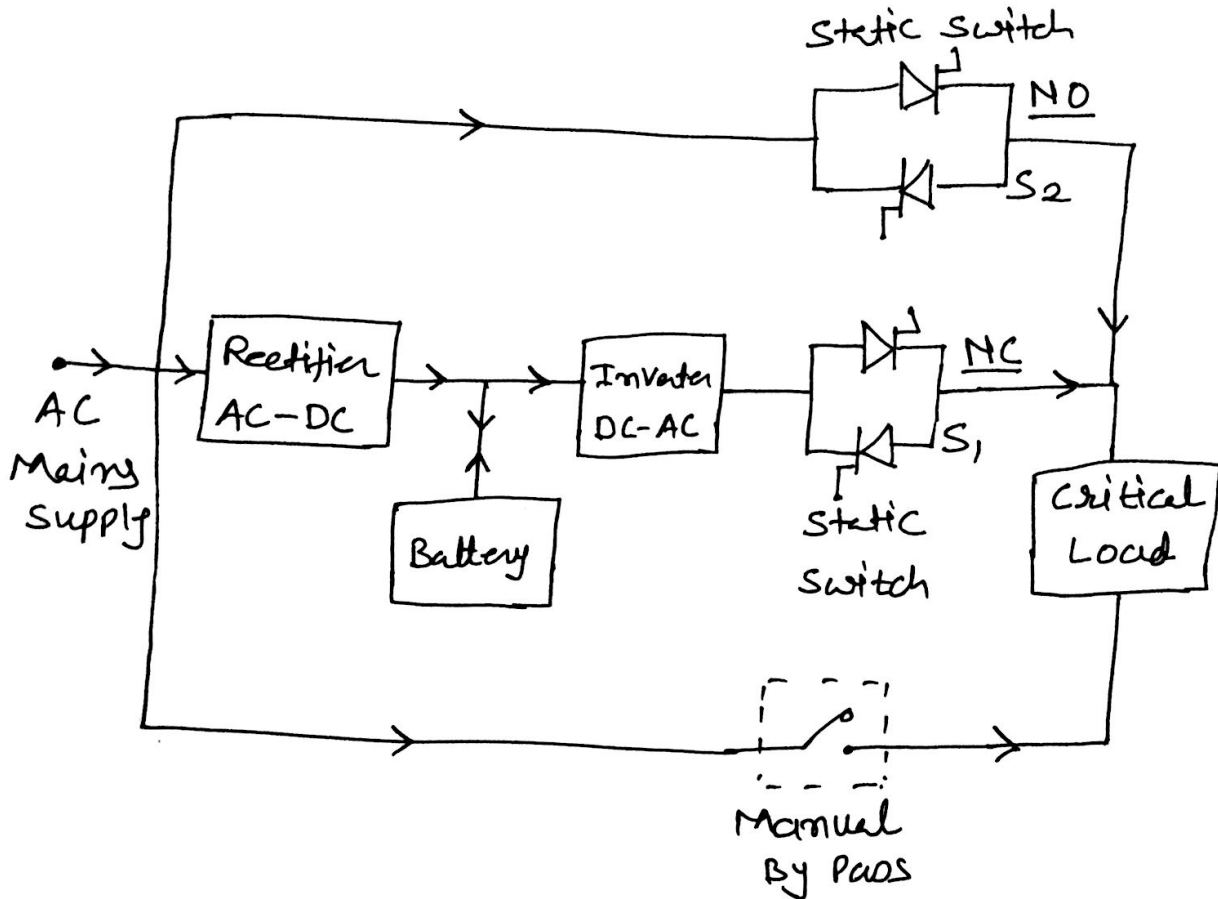
## OFF-Line UPS

↳ In OFF Line UPS, critical load is normally connected to AC mains supply.



Block diagram OFF-Line UPS


↳ OFF Line UPS consists of controlled Rectifier, Inverter, Battery, Battery charging ckt, two static switch and a manual by pass switch.

↳ when AC main supply is available the critical load is supplied through static switch  $S_2$  which is normally ON (NO).



- ↳ When main supply is not available switch  $S_2$  is turned off and switch  $S_1$  is ON.
- ↳ The critical supply is connected to the inverter output.
- ↳ The inverter is supplied by a battery.
- ↳ During the period when AC main supply is available, battery is fully charged by a rectifier and a battery charger circuit.
- ↳ The static switch takes 4 to 5 ms of time to turn on & off, while mechanical contactor may take 30 to 50 ms of time for operation.
- ↳ Here in OFF line UPS the inverter runs only during the time when the supply failure occurs.
- ↳ During maintenance period manual bypass switch is used to supply the load when AC mains supply is available.

# ON Line UPS

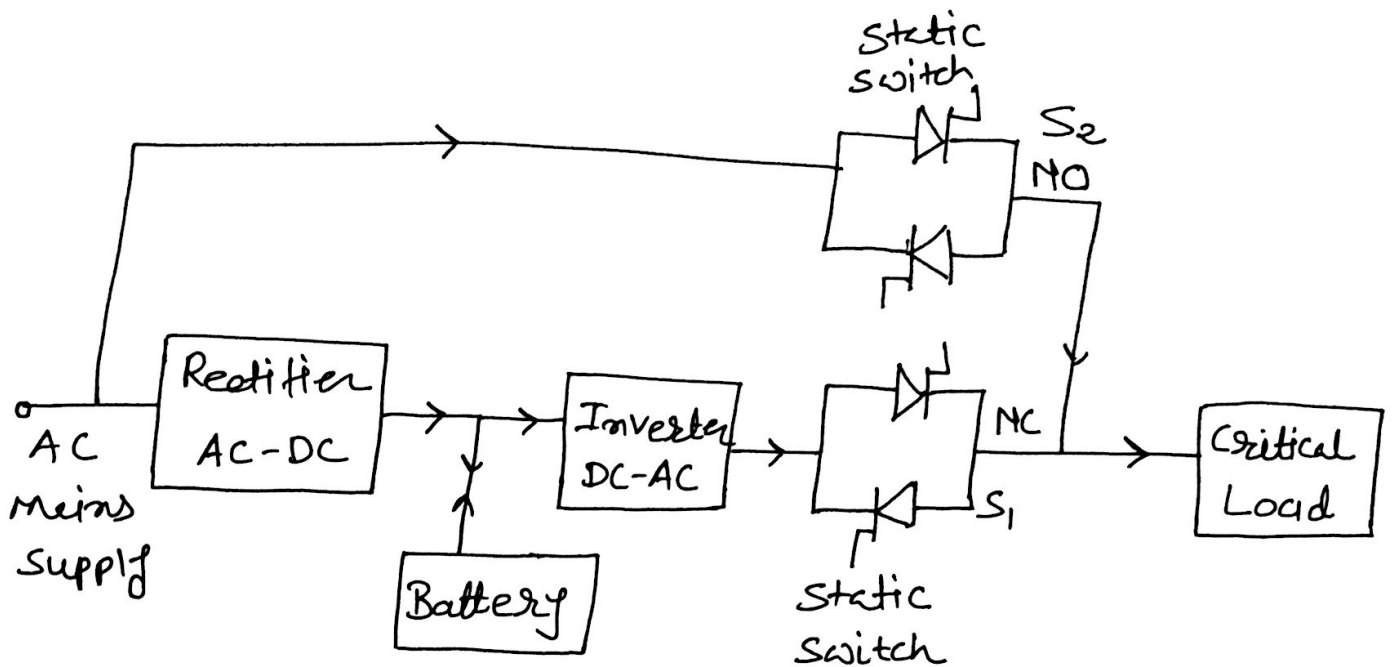


## Block - Diagram of ON Line UPS

- ↳ The inverter in on-line UPS operates continuously whether AC supply is available or not.
- ↳ The rectifier provides the necessary DC link voltage and charge the battery is also.
- ↳ static switch  $S_1$  is Normally close and  $S_2$  is normally open.
- ↳ The inverter can be used to improve the power quality.
- ↳ The inverter can be used to protect the load from transients, voltage variation, frequency change.


↳ The inverter is operated at fundamental output frequency with proper PWM scheme.

↳ There are some arrangements by which battery is isolated during main power is available.

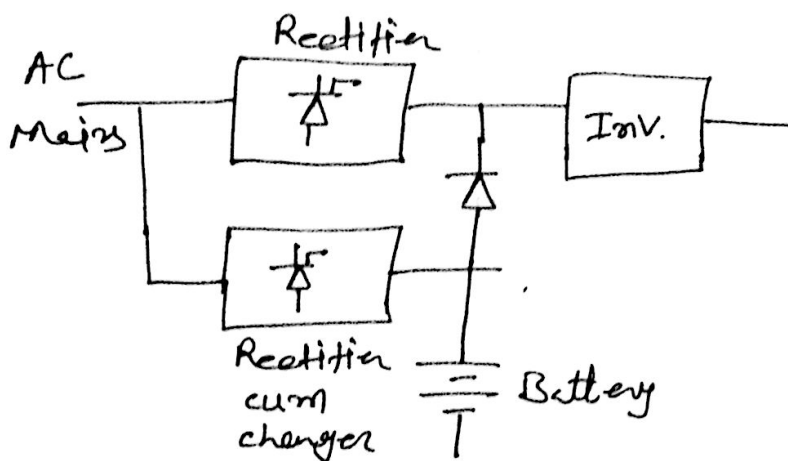↳ There may be SCR or Diode to control the battery power



## Line Interactive UPS

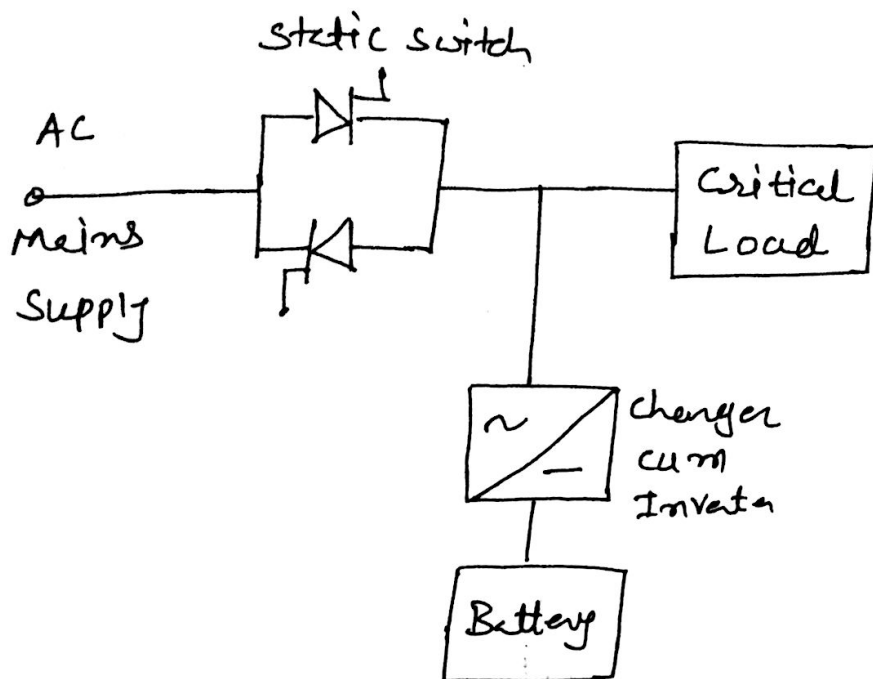

Block Diagram of Line Interactive UPS

- ↳ There is only one static switch provided in line interactive UPS.
- ↳ During the <sup>time</sup> AC mains supply is available critical load is supplied by AC mains.
- ↳ The Battery is charged with a charger cum inverter circuit.
- ↳ When the AC mains supply fails ~~and~~ the battery supplies the inverter and supplies critical load.

↳ The static switch is off during this ~~top~~ time.

↳ The system is simple and economical.

↳ If some fault occurs in charger then the whole system fails.


↳ The output of inverter varies with load current and battery voltage.

↳

# AC Power Supplies
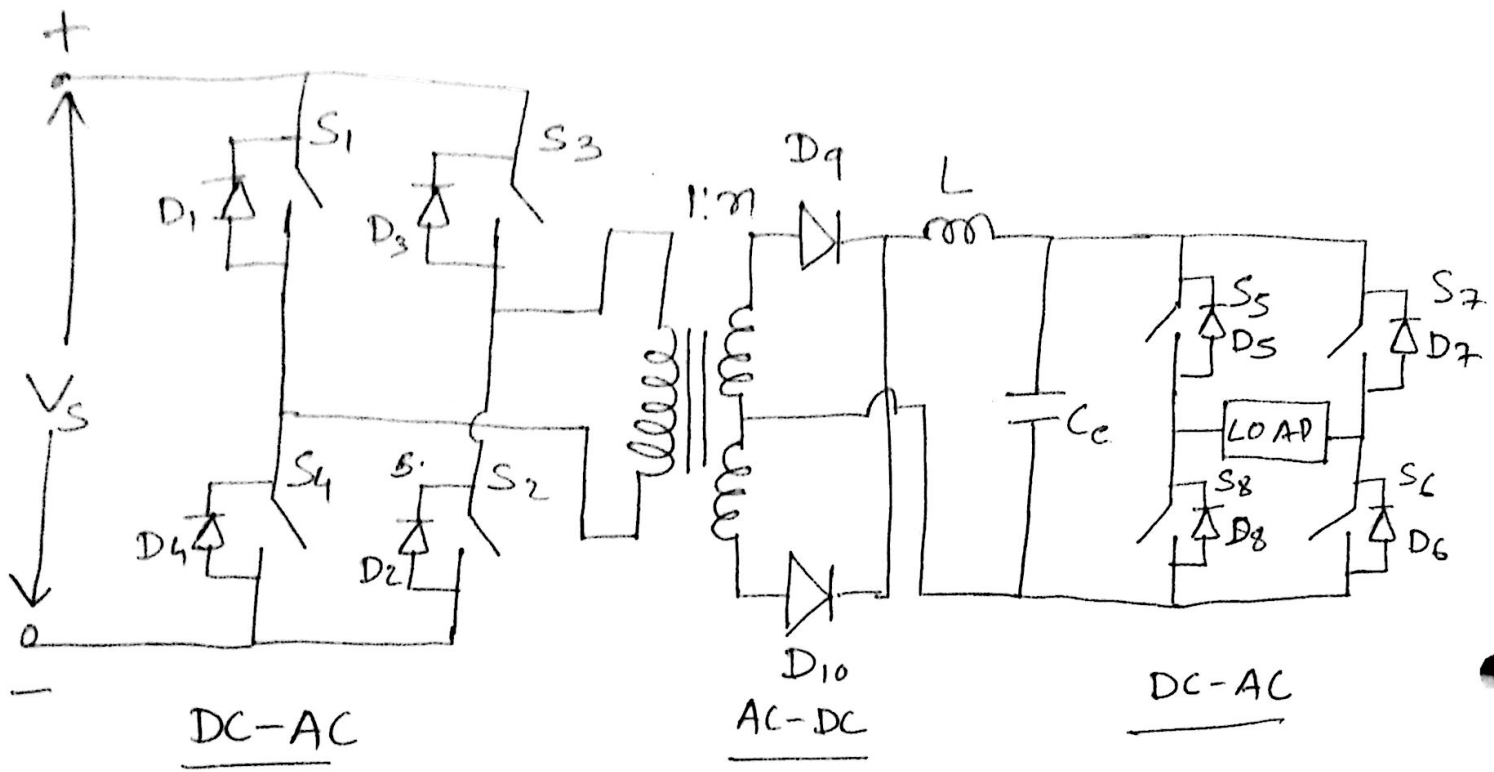
## Switched Mode AC Power supply

- ↳ The switched mode AC power supply consists of 3 stage conversion
- ↳ DC to AC, AC to DC and DC to AC.
- ↳ There are two inverters and a Buck converter.
- ↳ The input side inverter operates with a PWM control at a very high frequency.
- ↳ By increasing the frequency of inverter, the size of the transformer reduces.
- ↳ Also the DC filter component at the input of outside filter reduces.
- ↳ Hence the size of inverter power supply reduces.
- ↳ The output side inverter operates at output frequency.



↳ As shown above